



Multi-cycle Processor (Computer Organization: Chapter 4)



Yanyan Shen
**Department of Computer Science
and Engineering**

Recap: A Summary of Control Signals

inst Register Transfer

ADD $R[rd] \leftarrow R[rs] + R[rt];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{RegB}, ALUctr = \text{"add"}, \text{RegDst} = rd, \text{RegWr}, nPC_sel = \text{"+4"}$

SUB $R[rd] \leftarrow R[rs] - R[rt];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{RegB}, ALUctr = \text{"sub"}, \text{RegDst} = rd, \text{RegWr}, nPC_sel = \text{"+4"}$

ORi $R[rt] \leftarrow R[rs] + \text{zero_ext}(\text{Imm16});$ $PC \leftarrow PC + 4$

$ALUsrc = \text{Im}, \text{Extop} = \text{"Z"}, ALUctr = \text{"or"}, \text{RegDst} = rt, \text{RegWr}, nPC_sel = \text{"+4"}$

LOAD $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{Im}, \text{Extop} = \text{"Sn"}, ALUctr = \text{"add"},$
 $\text{MemtoReg}, \text{RegDst} = rt, \text{RegWr}, nPC_sel = \text{"+4"}$


STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] \leftarrow R[rs];$ $PC \leftarrow PC + 4$

$ALUsrc = \text{Im}, \text{Extop} = \text{"Sn"}, ALUctr = \text{"add"}, \text{MemWr}, nPC_sel = \text{"+4"}$

BEQ $\text{if } (R[rs] == R[rt]) \text{ then } PC \leftarrow PC + \text{sign_ext}(\text{Imm16}) \parallel 00 \text{ else } PC \leftarrow PC + 4$

$nPC_sel = \text{"Br"}, ALUctr = \text{"sub"}$

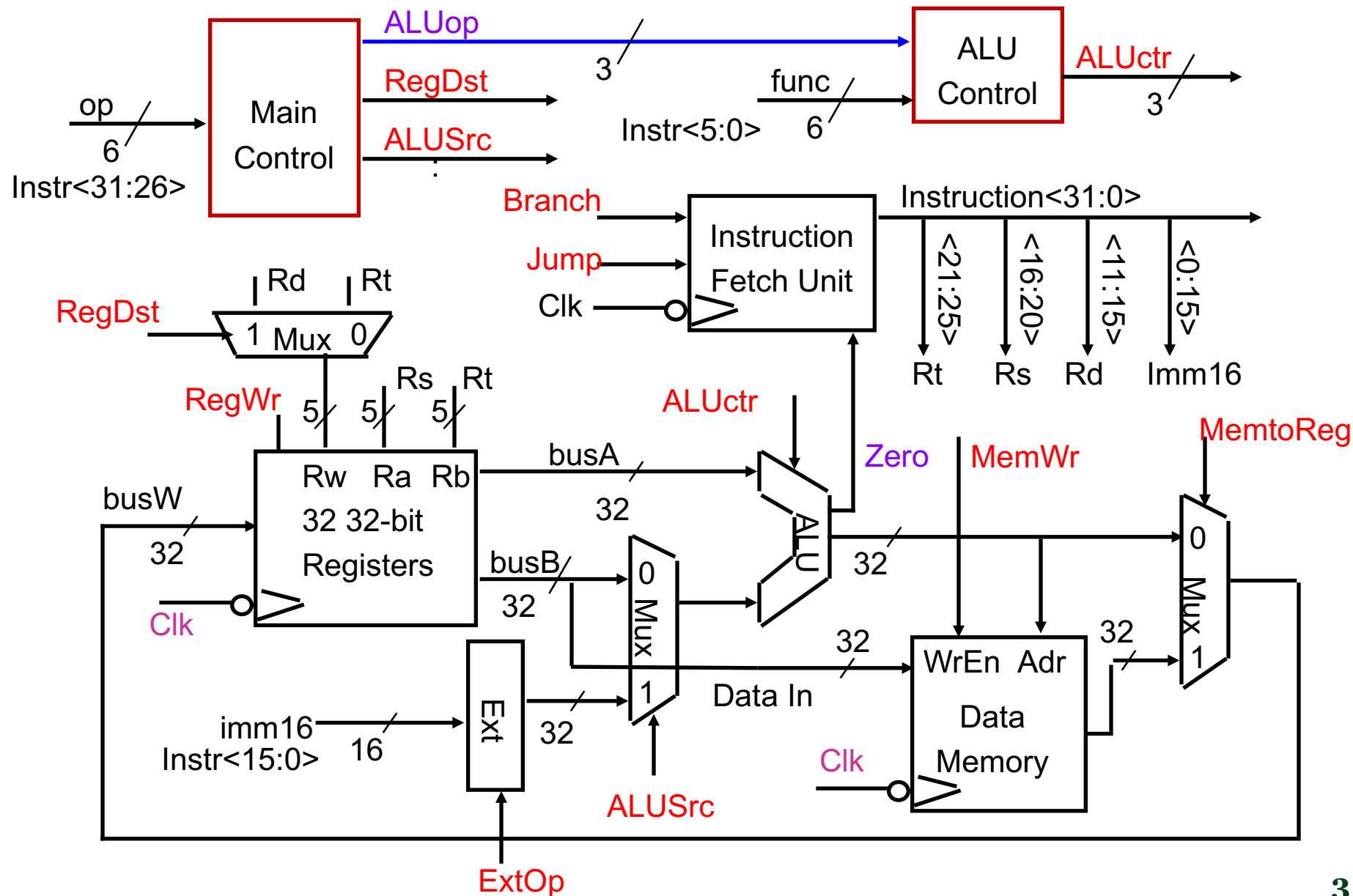
The Complete Single Cycle Data Path with Control



Creating a Single Datapath from the Parts

- ❑ Assemble the datapath segments and add control lines and multiplexors as needed
- ❑ **Single cycle** design – fetch, decode and execute each instructions in **one** clock cycle
 - no datapath resource can be used more than once per instruction, so some must be duplicated (e.g., separate Instruction Memory and Data Memory, several adders)
 - multiplexors needed at the input of shared elements with control lines to do the selection
 - write signals to control writing to the Register File and Data Memory
- ❑ Cycle time is determined by length of the longest path

Clocking Methodology

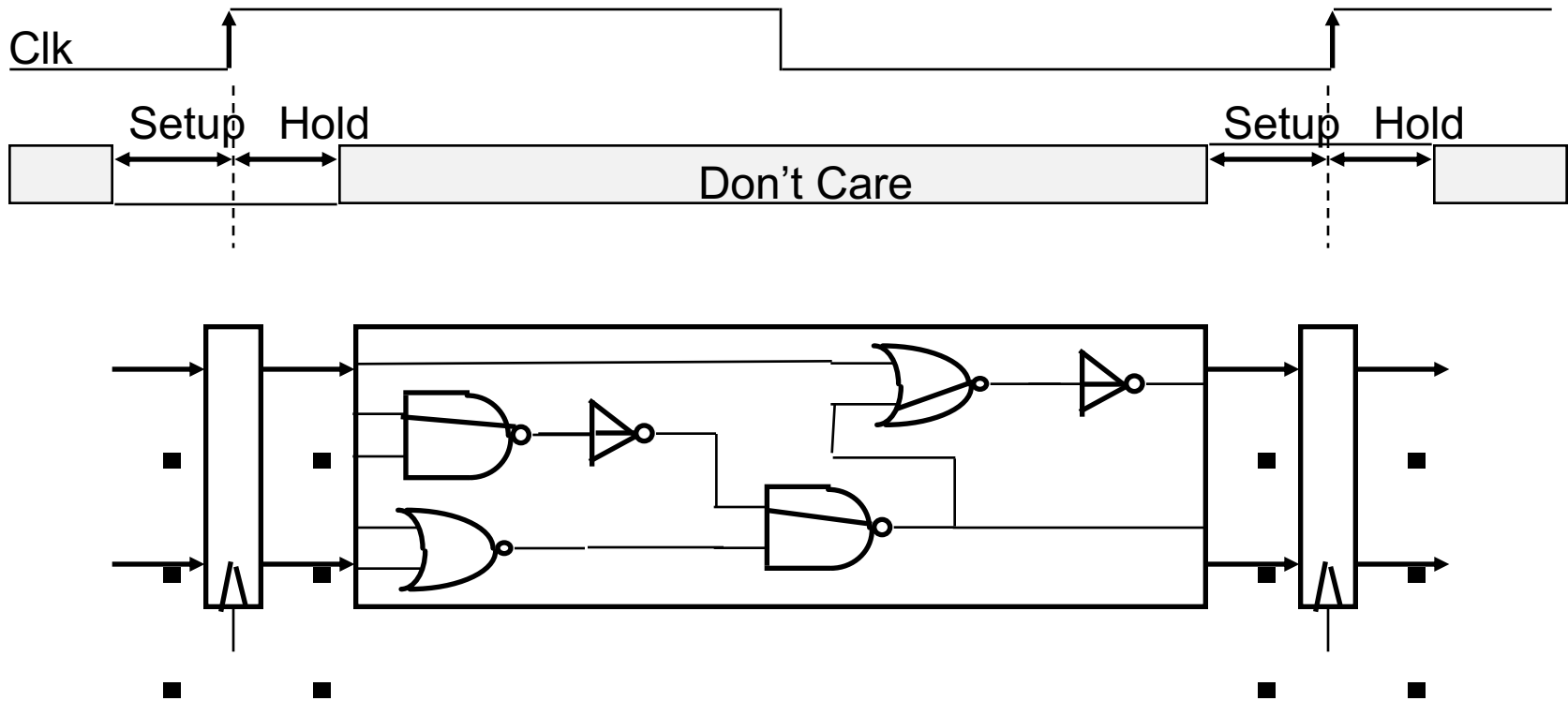

- ❑ All storage elements are clocked by the same clock edge
- ❑ **Cycle Time** = CLK-to-Q + **Longest Delay Path** + Setup + Clock Skew

Instruction Critical Paths

❑ Calculate cycle time assuming negligible delays (for muxes, control unit, sign extend, PC access, shift left 2, wires, setup and hold times) except:


Instruction and Data Memory (200 ps)

ALU and adders (100 ps)


Register File access (reads or writes) (50 ps)

Instr.	I Mem	Reg Rd	ALU Op	D Mem	Reg Wr	Total
R-type	200	50	100	0	50	400
load	200	50	100	200	50	600
store	200	50	100	200		550
beq	200	50	100	0		350
jump	200					200

Fetch, R, and Memory Access Portions

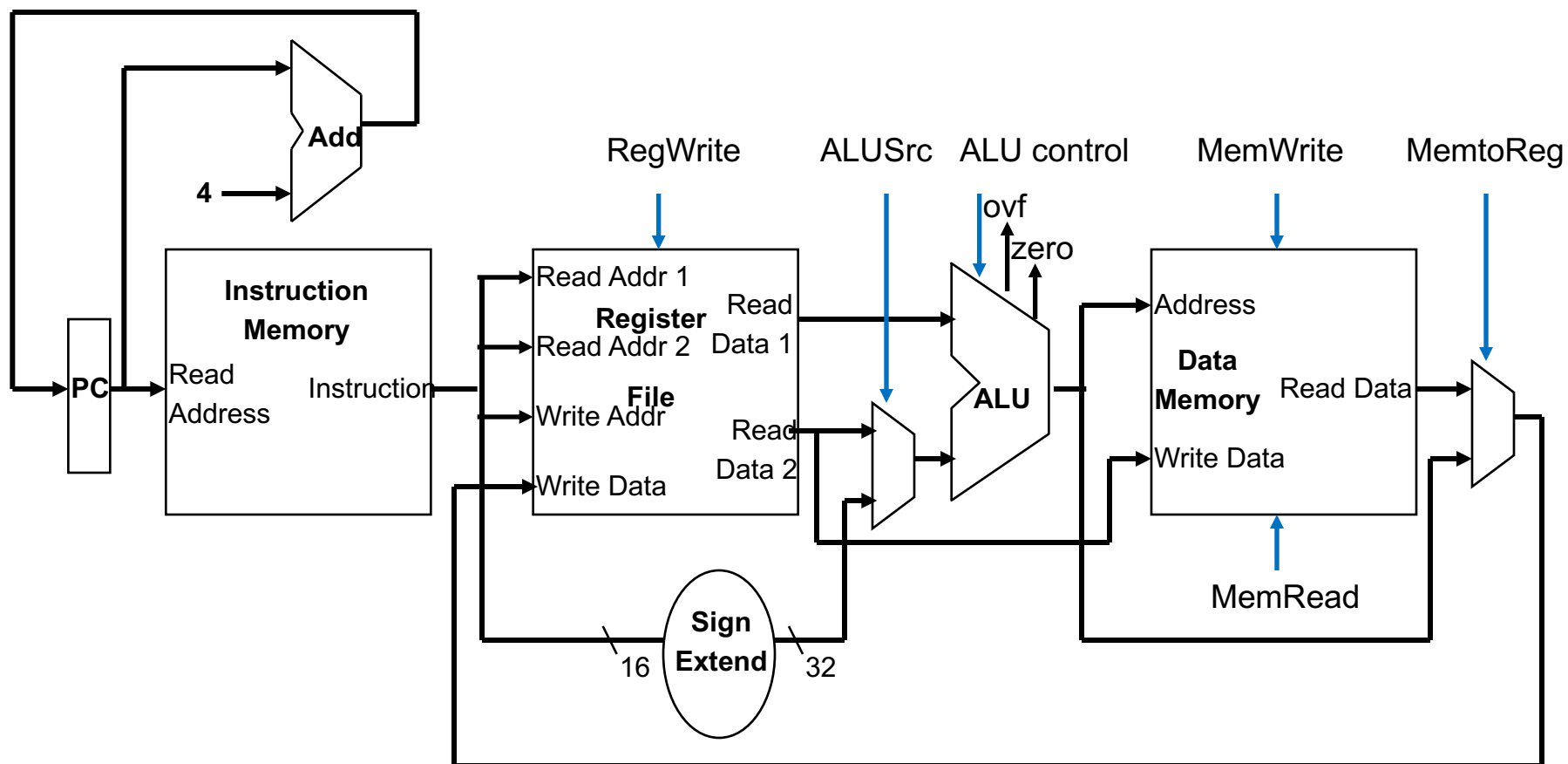

Time Delay for LW: Critical Path

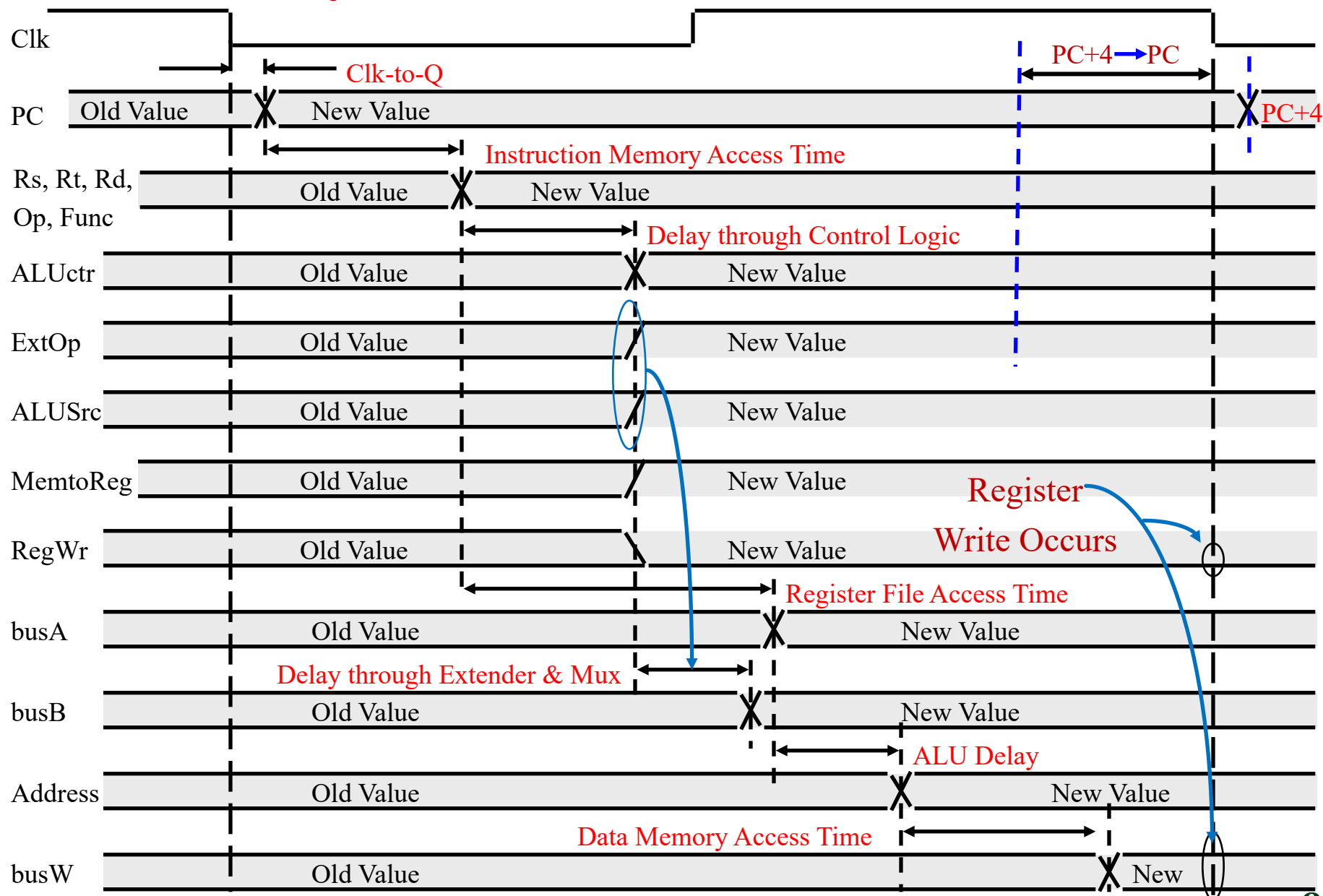


What's wrong with our CPI=1 processor?

Arithmetic & Logical



Load

 

← Critical Path →

Store




Branch



Single Cycle Disadvantages & Advantages

 - ❑ Uses the clock cycle inefficiently – the clock cycle must be timed to accommodate the **slowest** instruction
 - especially problematic for more complex instructions like floating point multiply




- ❑ May be wasteful of area since some functional units (e.g., adders) must be duplicated since they can not be shared during a clock cycle
- ❑ But is simple and easy to understand

Multicycle Implementation Overview


- ❑ Each instruction **step** takes 1 clock cycle
 - Therefore, an instruction takes **more than 1 clock cycle** to complete
- ❑ Not every instruction takes the **same** number of clock cycles to complete
- ❑ Multicycle implementations allow
 - faster clock rates
 - different instructions to take a different number of clock cycles
 - functional units to be used more than once per instruction as long as they are used on different clock cycles, as a result
 - only need one memory
 - only need one ALU/adder

The Multicycle Datapath – A High Level View

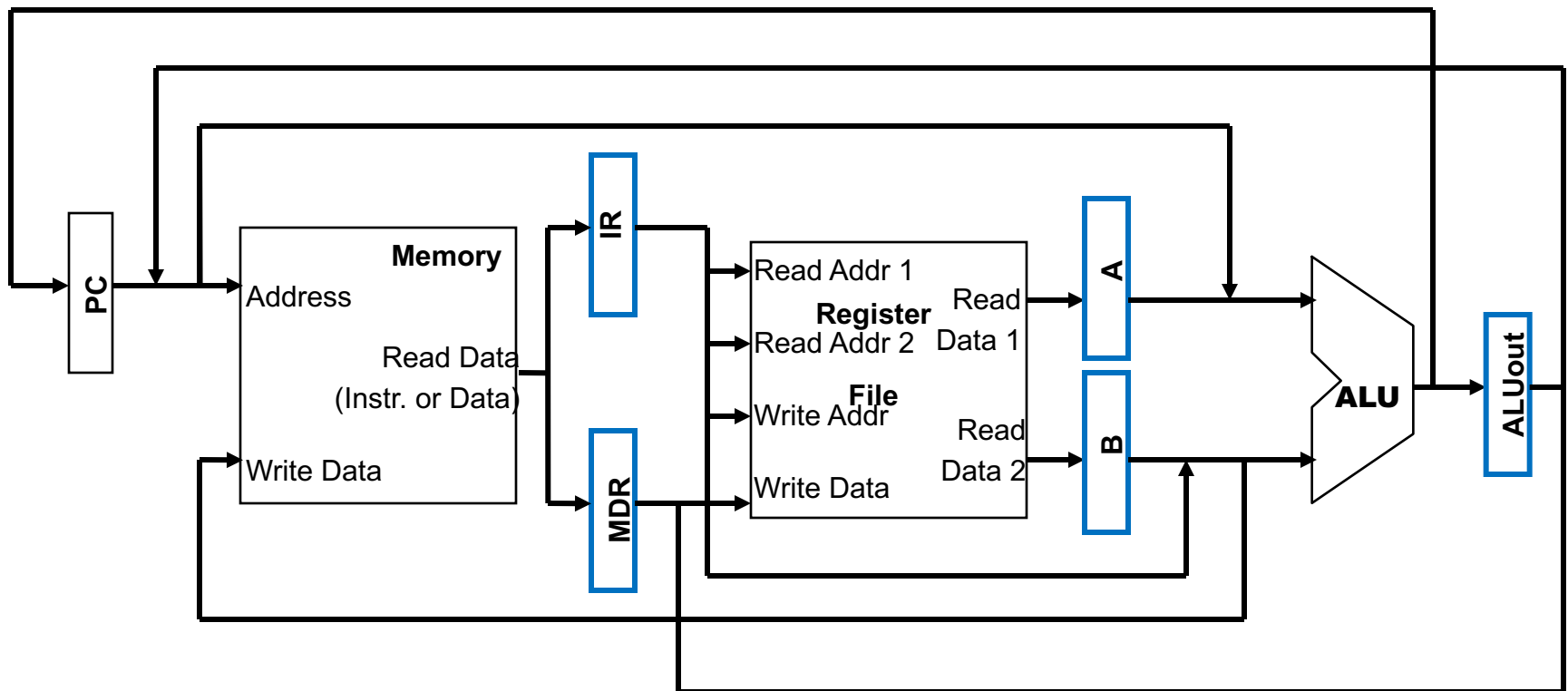- ❑ Registers have to be added after every major functional unit to hold the output value until it is used in a subsequent clock cycle




Clocking the Multicycle Datapath

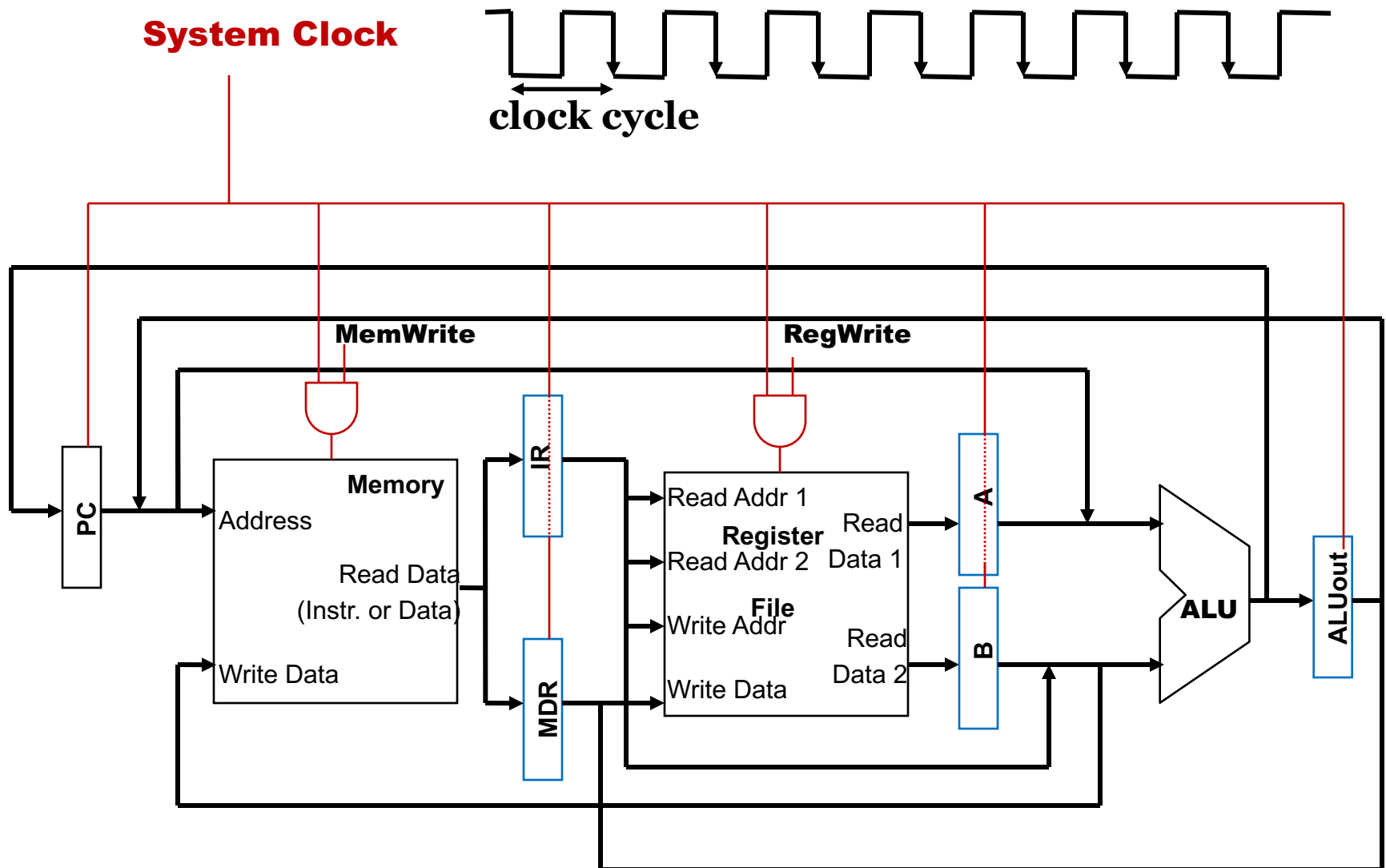

Our Multicycle Approach

- ❑ Break up the instructions into steps where each step takes a clock cycle while trying to
 - balance the amount of work to be done in each step
 - use only one major functional unit per clock cycle
- ❑ At the end of a clock cycle
 - Store values needed in a later clock cycle by the **current** instruction in a state element (internal register not visible to the programmer)
 - IR – Instruction Register
 - MDR – Memory Data Register
 - A and B – Register File read data registers
 - ALUout – ALU output register
 - All (except IR) hold data only between a pair of adjacent clock cycles (so they don't need a write control signal)
 - Data used by subsequent instructions are stored in programmer visible state elements (i.e., Register File, PC, or Memory)

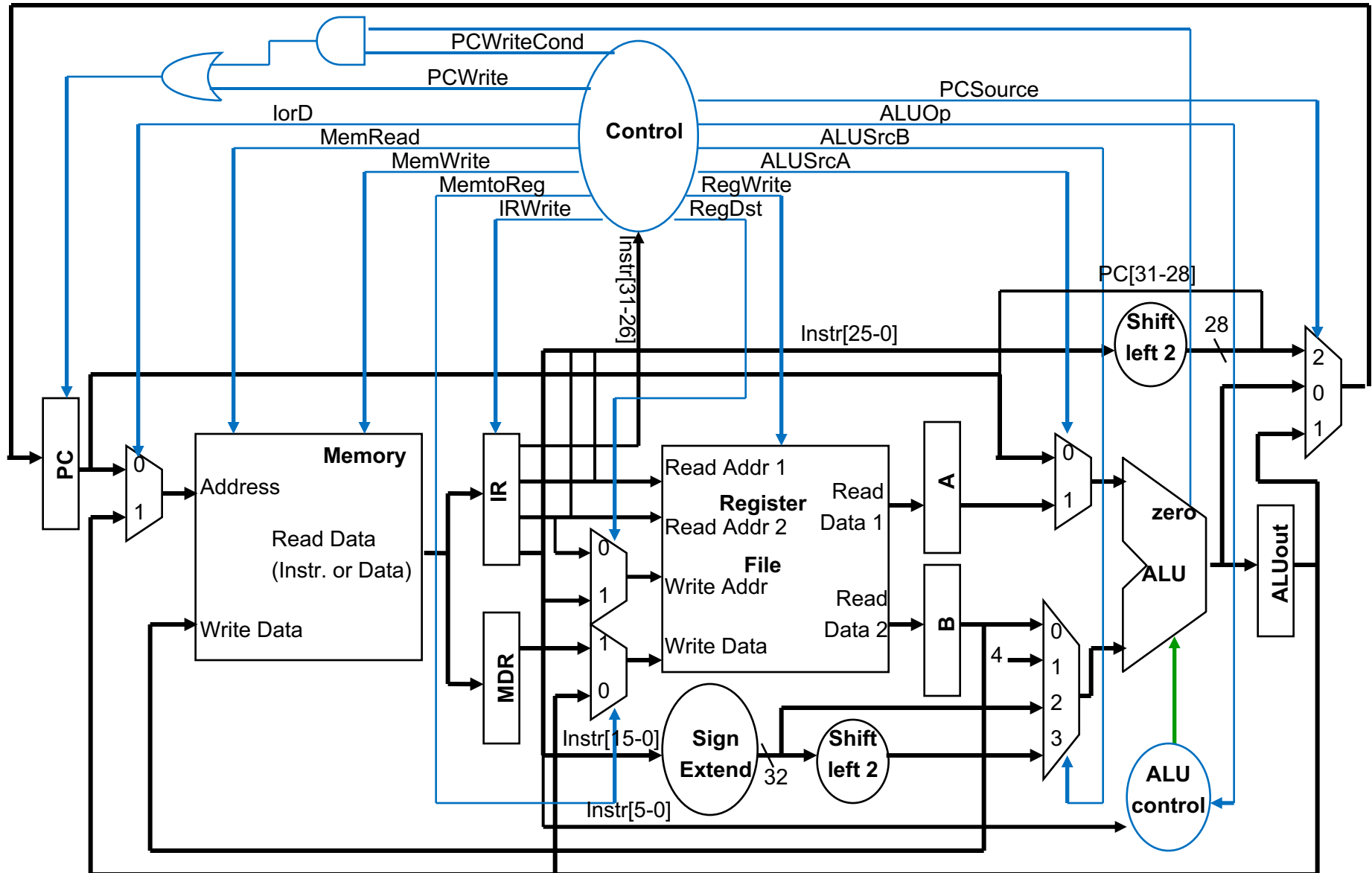The Complete Multicycle Datapath with Control



Our Multicycle Approach, con't

- ❑ Reading from or writing to any of the internal registers, Register File, or the PC occurs (quickly) at the beginning (for read) or the end of a clock cycle (for write)
- ❑ Reading from the Register File takes ~50% of a clock cycle since it has additional control and access overhead (but reading can be done in parallel with decode)
- ❑ Had to add multiplexors in front of several of the functional unit input ports (e.g., Memory, ALU) because they are now shared by different clock cycles and/or do multiple jobs
- ❑ All operations occurring in one clock cycle occur in parallel
 - This limits us to one ALU operation, one Memory access, and one Register File access per clock cycle

Five Instruction Steps

- 1) Instruction Fetch
- 2) Instruction Decode and Register Fetch
- 3) R-type Instruction Execution, Memory Read/Write Address Computation, Branch Completion, or Jump Completion
- 4) Memory Read Access, Memory Write Completion or R-type Instruction Completion
- 5) Memory Read Completion (**Write Back**)

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

RTL for Instructions

❑ Common Steps:

- Instr fetch $IR = Memory[PC];$
- PC Updating $PC = PC + 4;$

❑ Decode and Register reading


- $A = Reg[IR[25-21]];$
- $B = Reg[IR[20-16]];$

❑ Instruction Dependent operation

RTL Summary

Step	R-type	Mem Ref	Branch	Jump
Instr fetch	$\text{IR} = \text{Memory}[\text{PC}];$ $\text{PC} = \text{PC} + 4;$			
Decode	$\text{A} = \text{Reg}[\text{IR}[25-21]];$ $\text{B} = \text{Reg}[\text{IR}[20-16]];$ $\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2);$			
Execute	$\text{ALUOut} =$ $\text{A op B};$	$\text{ALUOut} =$ $\text{A} + \text{sign-extend}$ $(\text{IR}[15-0]);$	if $(\text{A} == \text{B})$ $\text{PC} =$ $\text{ALUOut};$	$\text{PC} =$ $\text{PC}[31-28]$ $ (\text{IR}[25-$ $0] \ll 2);$
Memory access	$\text{Reg}[\text{IR}[15$ $-11]] =$ $\text{ALUOut};$	$\text{MDR} =$ $\text{Memory}[\text{ALUOut}];$ or $\text{Memory}[\text{ALUOut}]$ $= \text{B};$		
Write- back		$\text{Reg}[\text{IR}[20-16]]$ $= \text{MDR};$		

Multi-cycle datapath

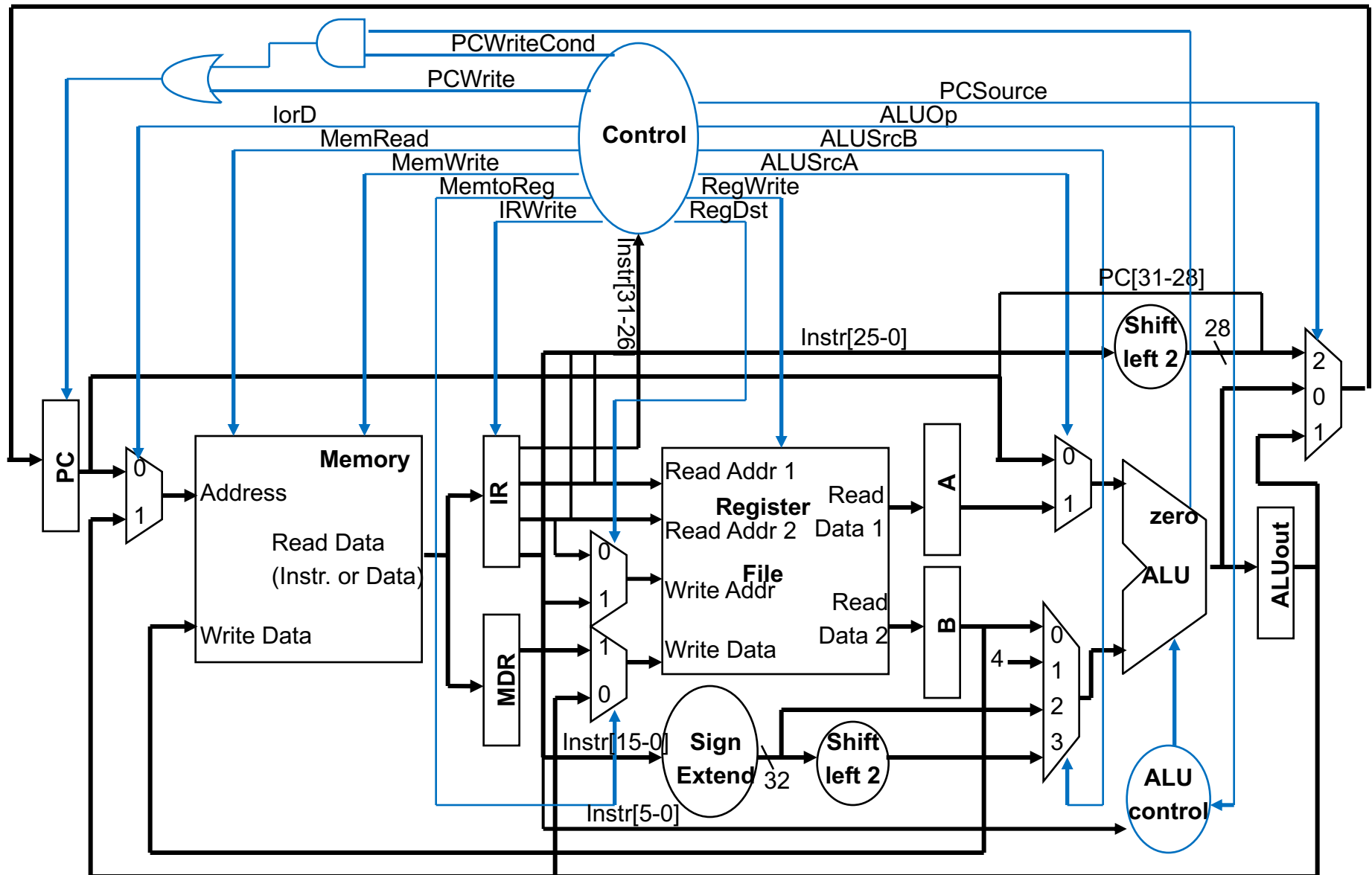

Step 1: Instruction Fetch


- ❑ Use PC to get instruction from the memory and put it in the Instruction Register
- ❑ Increment the PC by 4 and put the result back in the PC
- ❑ Can be described succinctly using the RTL "Register-Transfer Language"

```
IR = Memory[PC];
PC = PC + 4;
```


Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

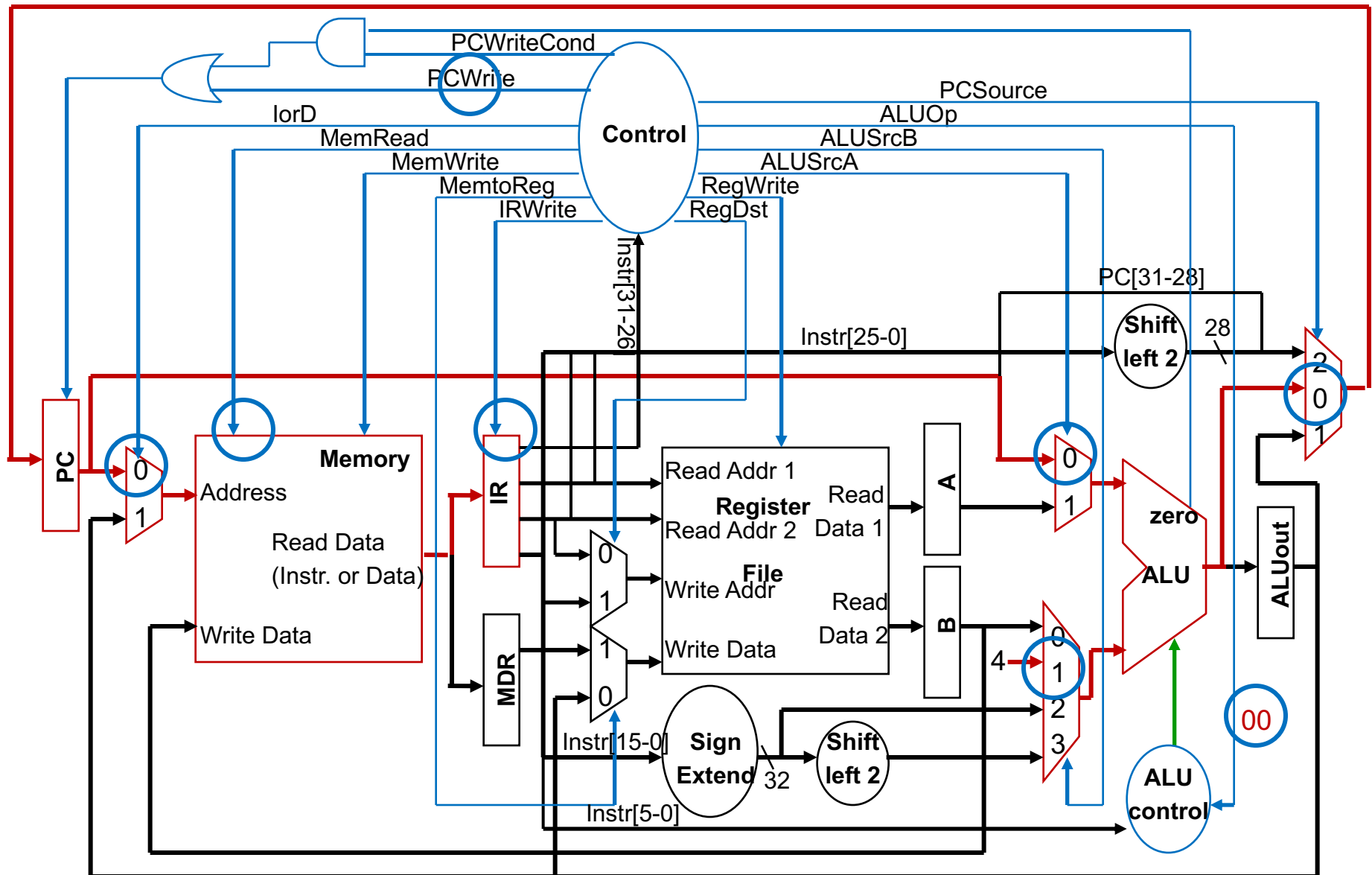Datapath Activity During Instruction Fetch



Fetch Control Signals Settings

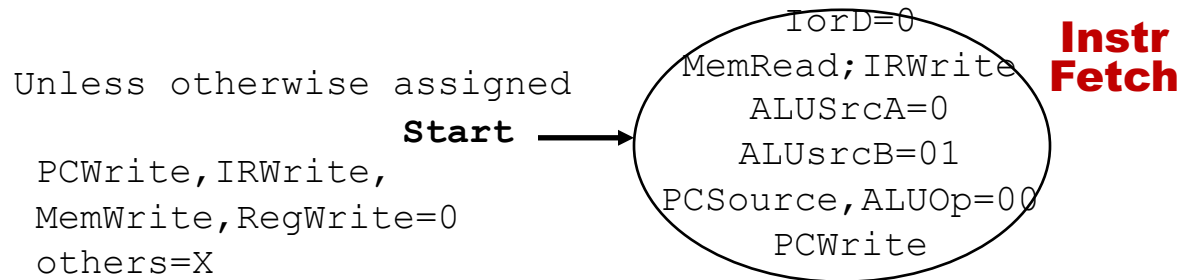

Step 2: Instruction Decode and Register Fetch

- ❑ Don't know what the instruction is yet, so can only
 - Read registers *rs* and *rt* in case we need them
 - Compute the branch address in case the instruction is a branch

❑ The RTL:


$A = \text{Reg}[\text{IR}[25-21]];$

$B = \text{Reg}[\text{IR}[20-16]];$


$\text{ALUOut} = \text{PC} + (\text{sign-extend}(\text{IR}[15-0]) \ll 2);$

- ❑ Note we aren't setting any control lines based on the instruction (since we don't know what it is (the control logic is busy "**decoding**" the op code bits))

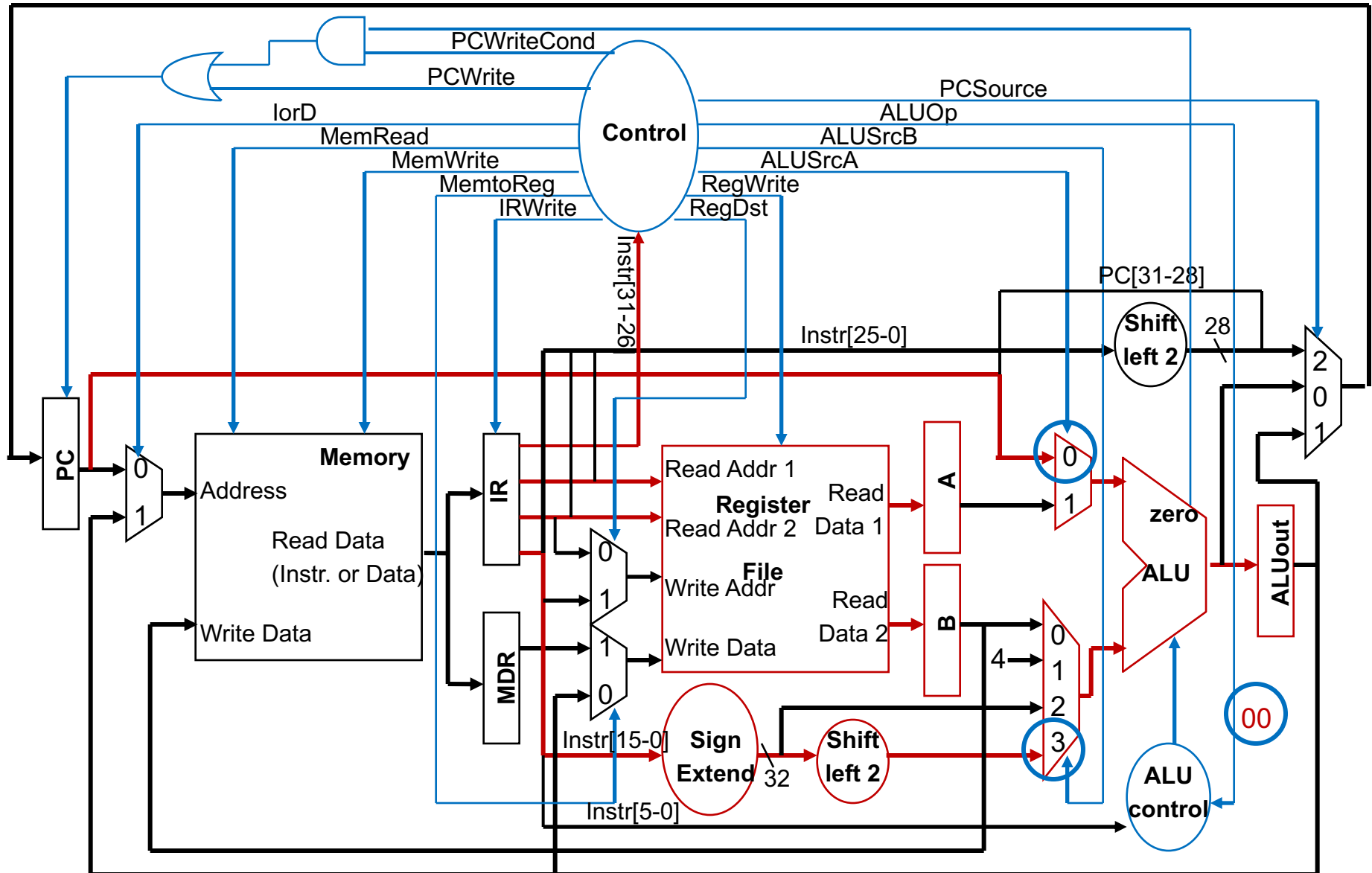Datapath Activity During Instruction Decode



Decode Control Signals Settings

 

Step 3 Instruction Dependent Operations

- ALU is performing one of four functions, based on instruction type

- Memory reference (`lw` and `sw`):

$$\text{ALUOut} = A + \text{sign-extend}(\text{IR}[15-0]);$$

- R-type:

$$\text{ALUOut} = A \text{ op } B;$$


- Branch:

$$\text{if } (A == B) \text{ PC} = \text{ALUOut};$$


- Jump:

$$\text{PC} = \text{PC}[31-28] \parallel (\text{IR}[25-0] \ll 2);$$


Datapath Activity During lw & sw Execute

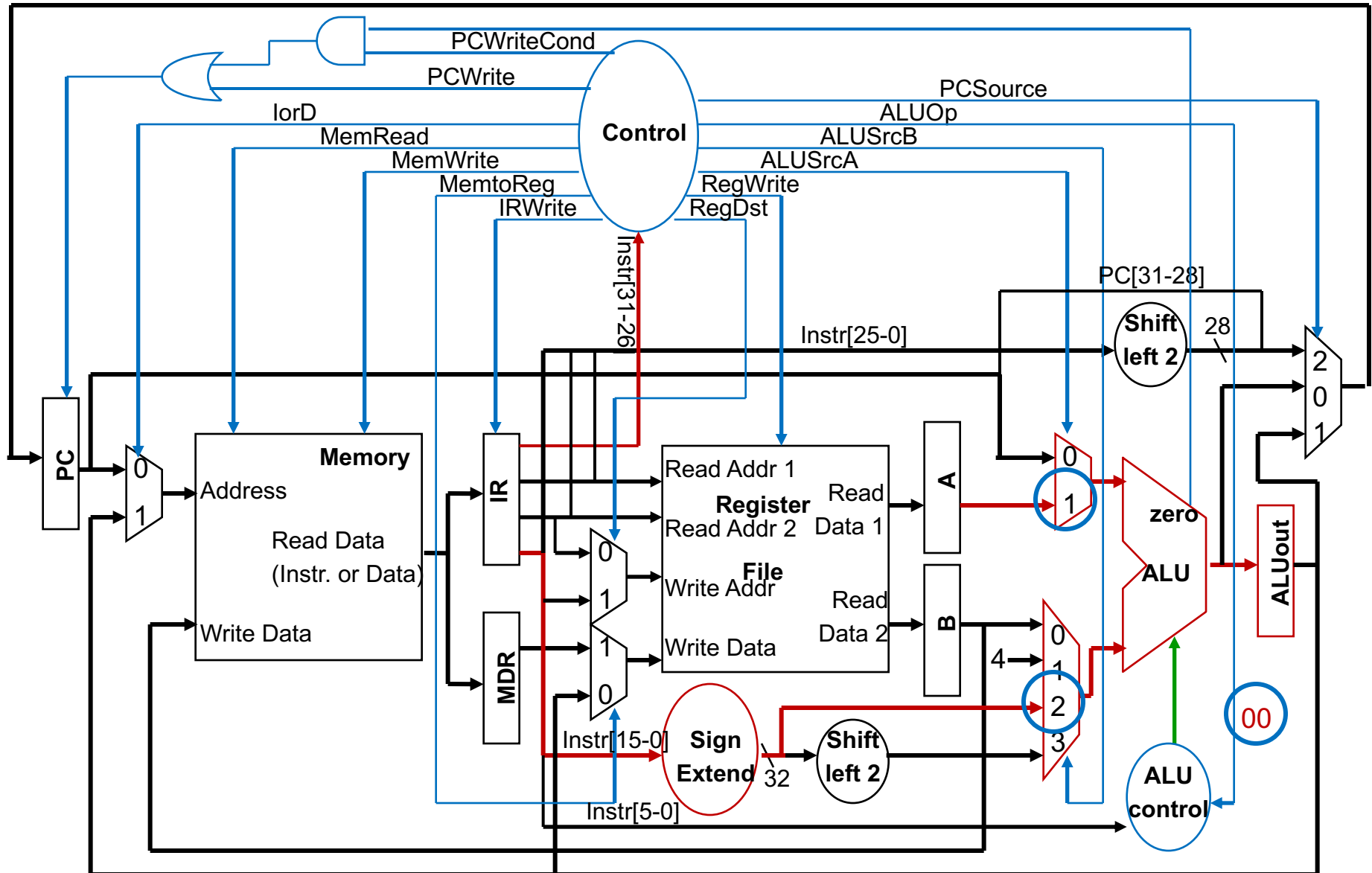


Datapath Activity During R-type Execute

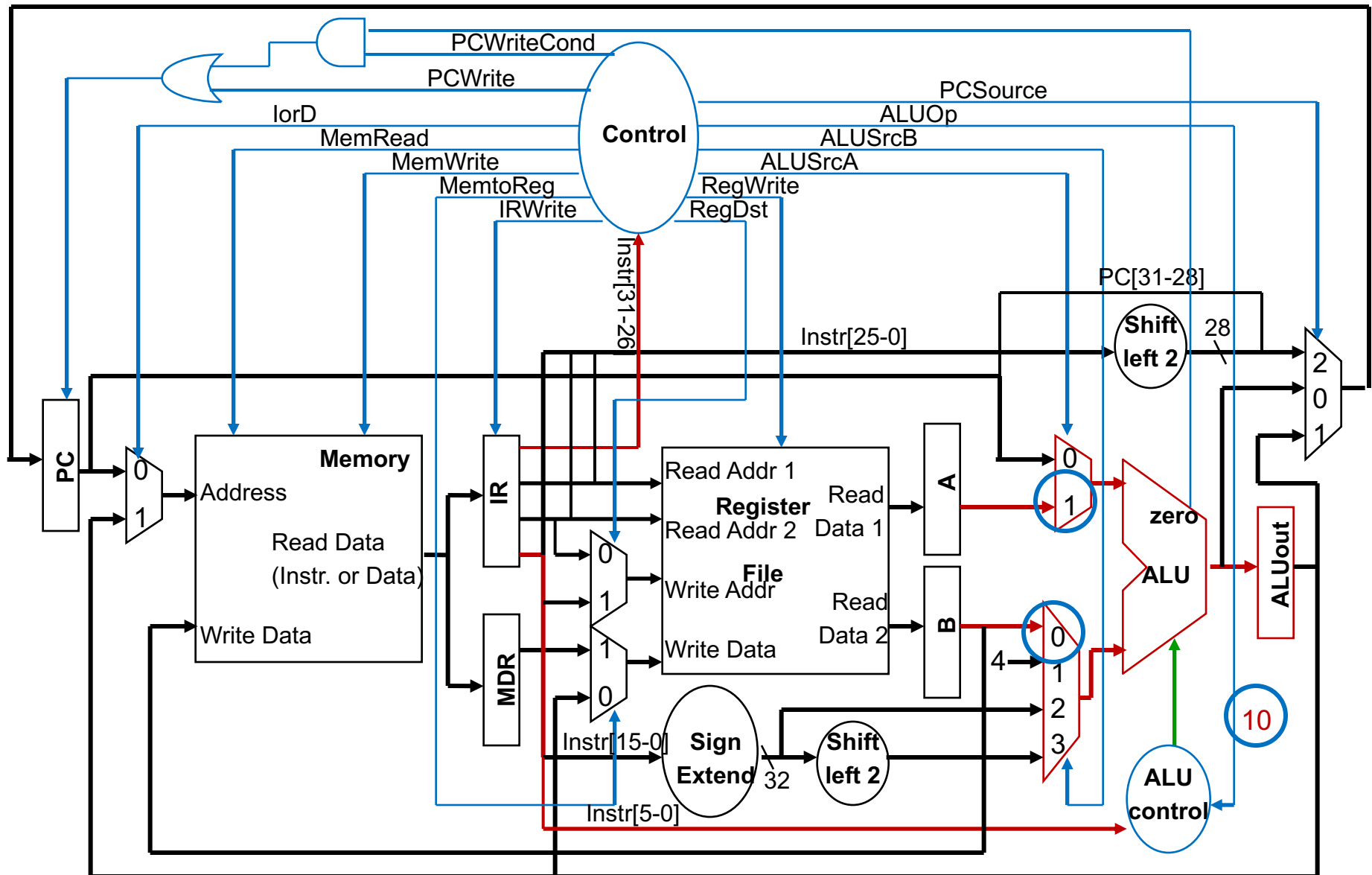


Datapath Activity During beq Execute

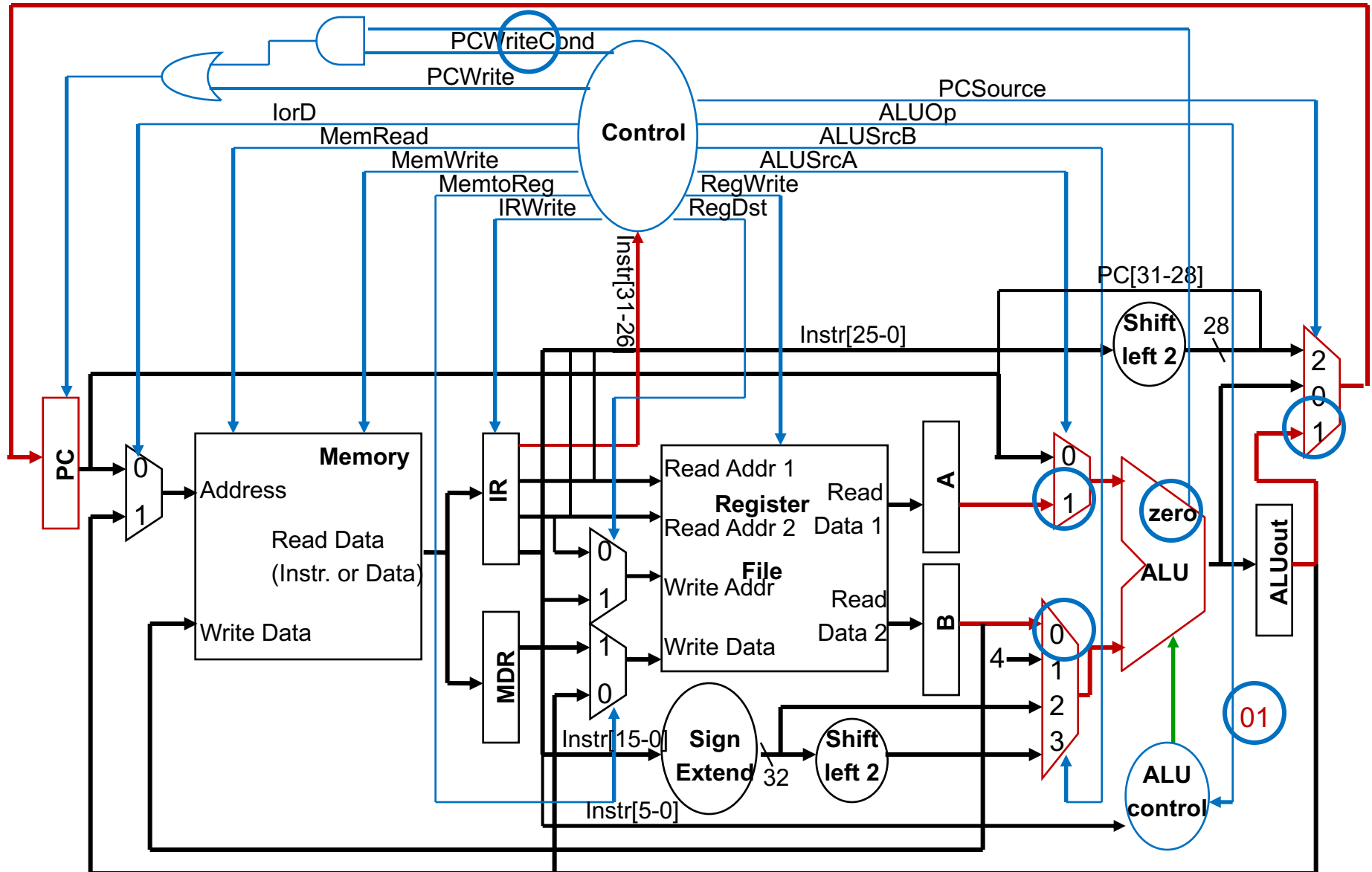

Datapath Activity During j Execute

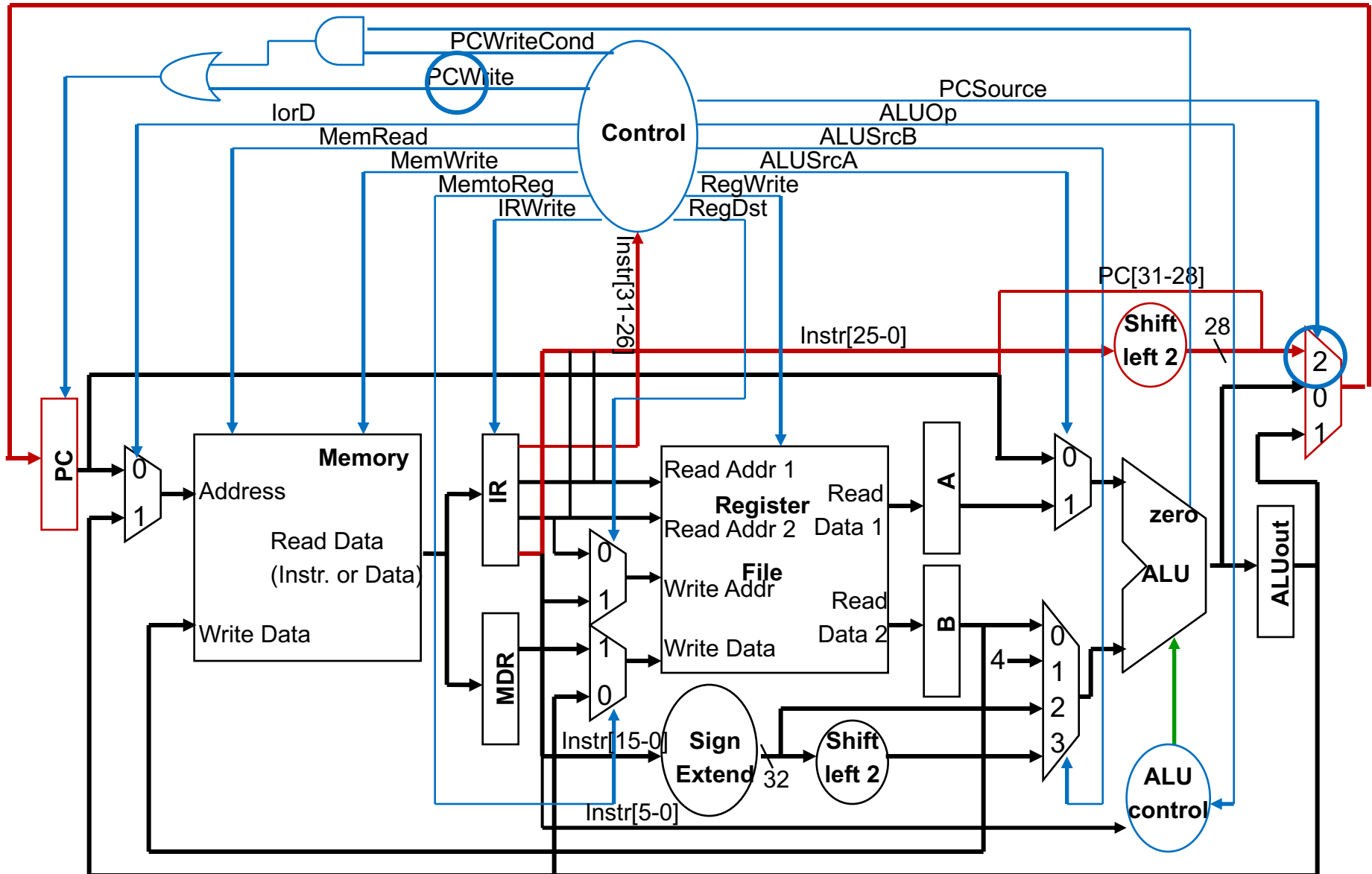

Execute Control Signals Settings

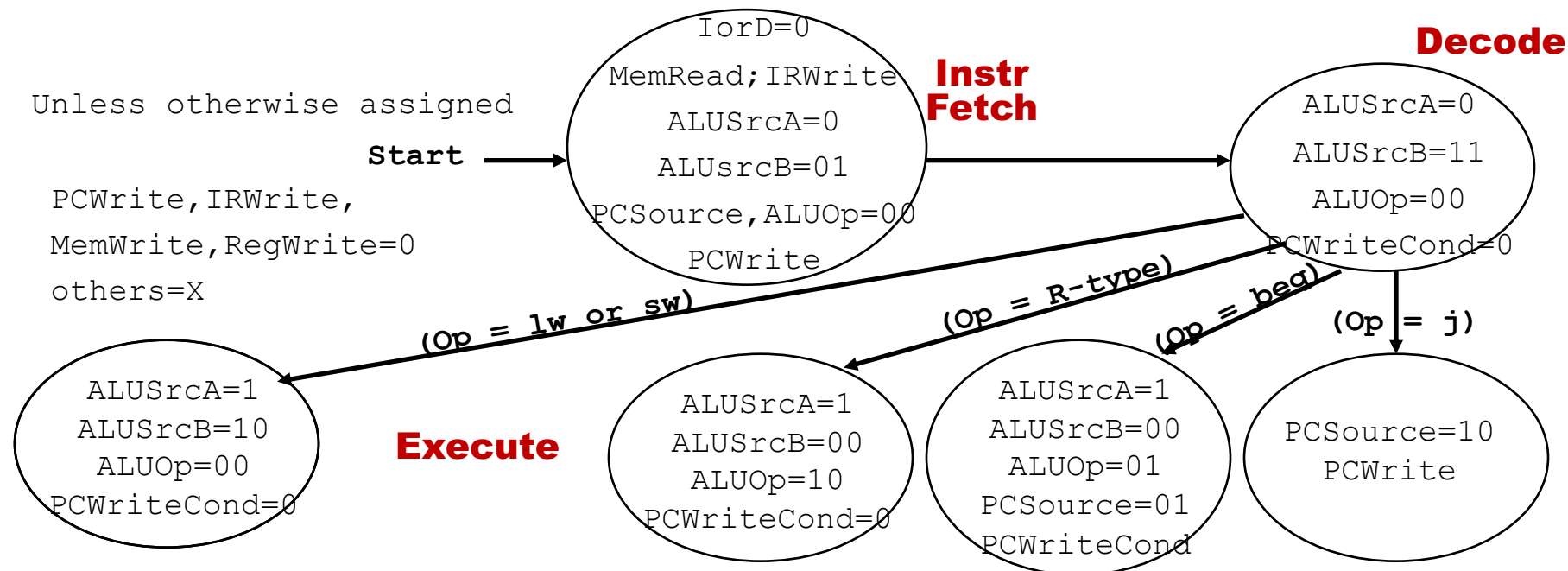

Step 4 (also instruction dependent)

- Memory reference:

`MDR = Memory[ALUOut];` `-- lw`

or


`Memory[ALUOut] = B;` `-- sw`

- R-type instruction completion


`Reg[IR[15-11]] = ALUOut;`

- Remember, the register write actually takes place at the **end** of the cycle on the clock edge

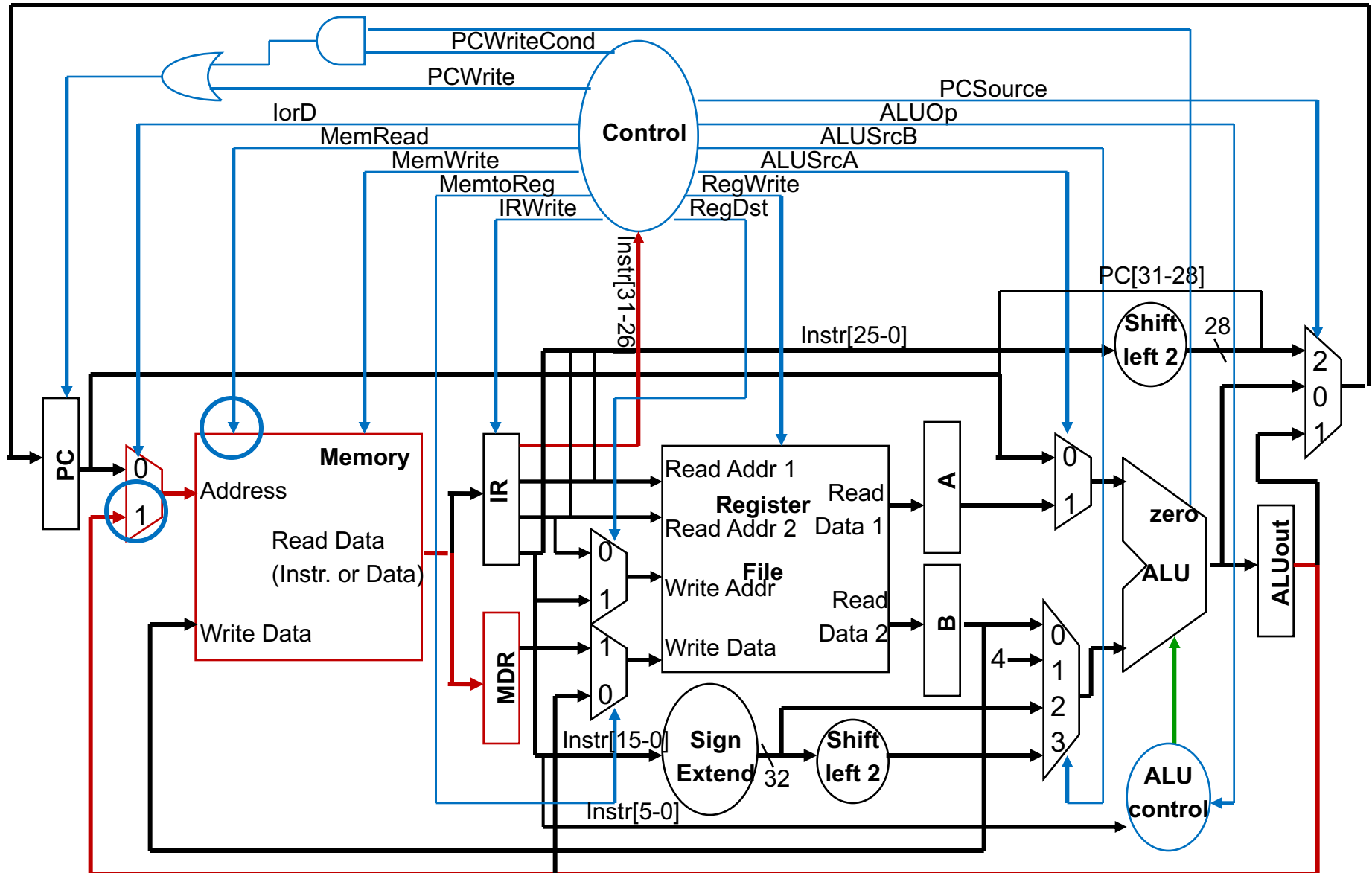
Datapath Activity During 1w Memory Access



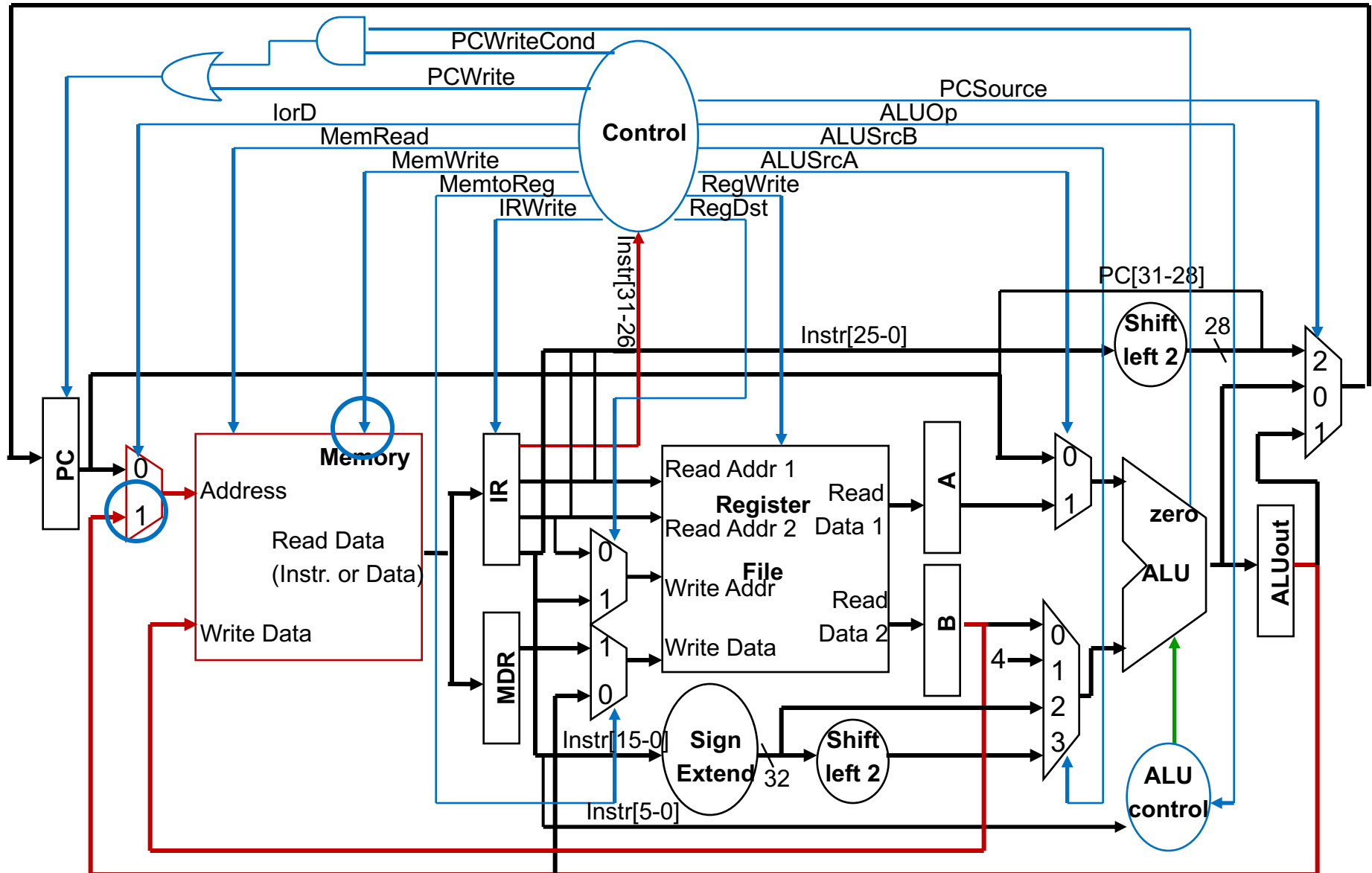
Datapath Activity During sw Memory Access



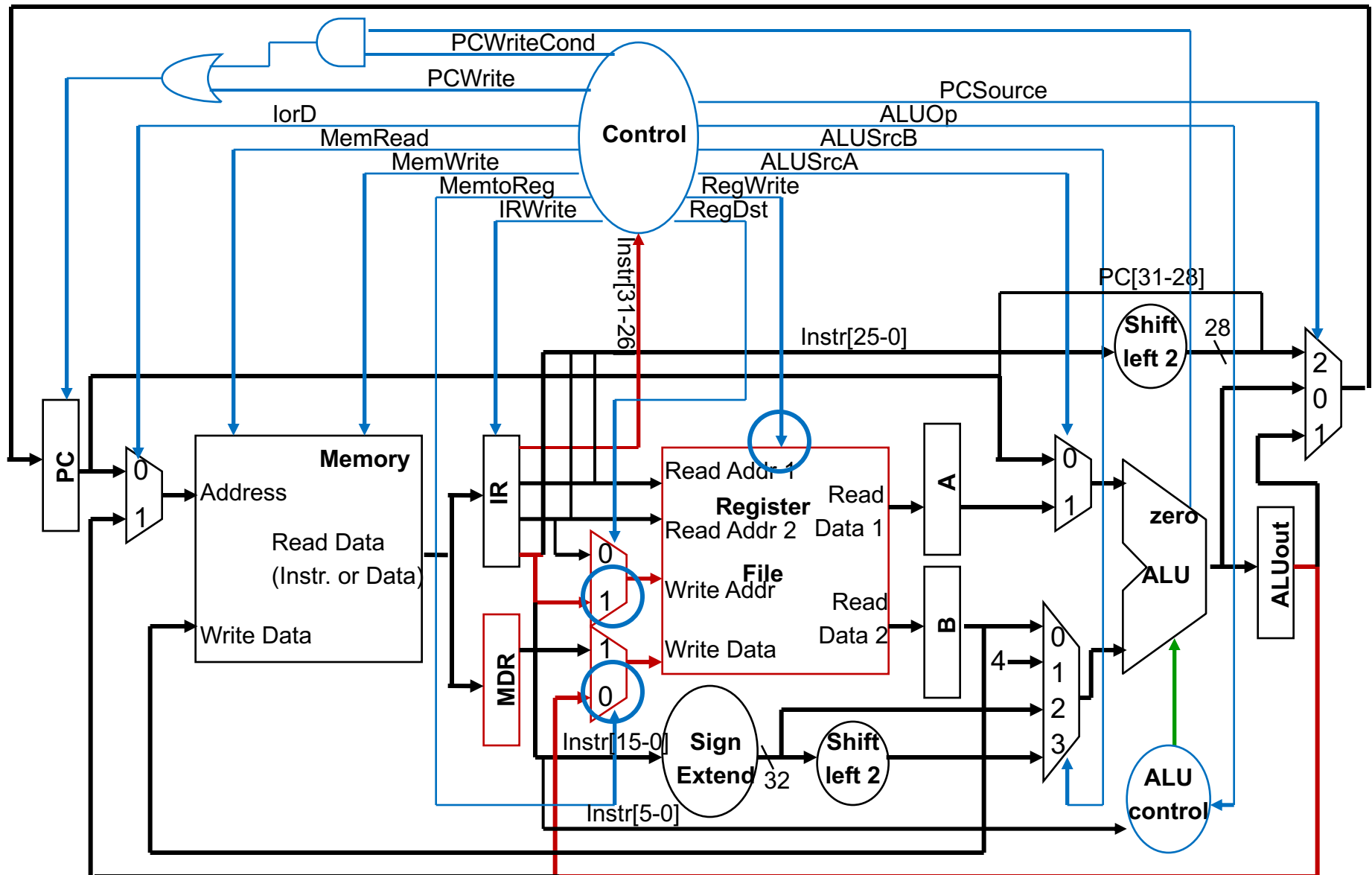Datapath Activity During R-type Completion



Memory Access Control Signals Settings

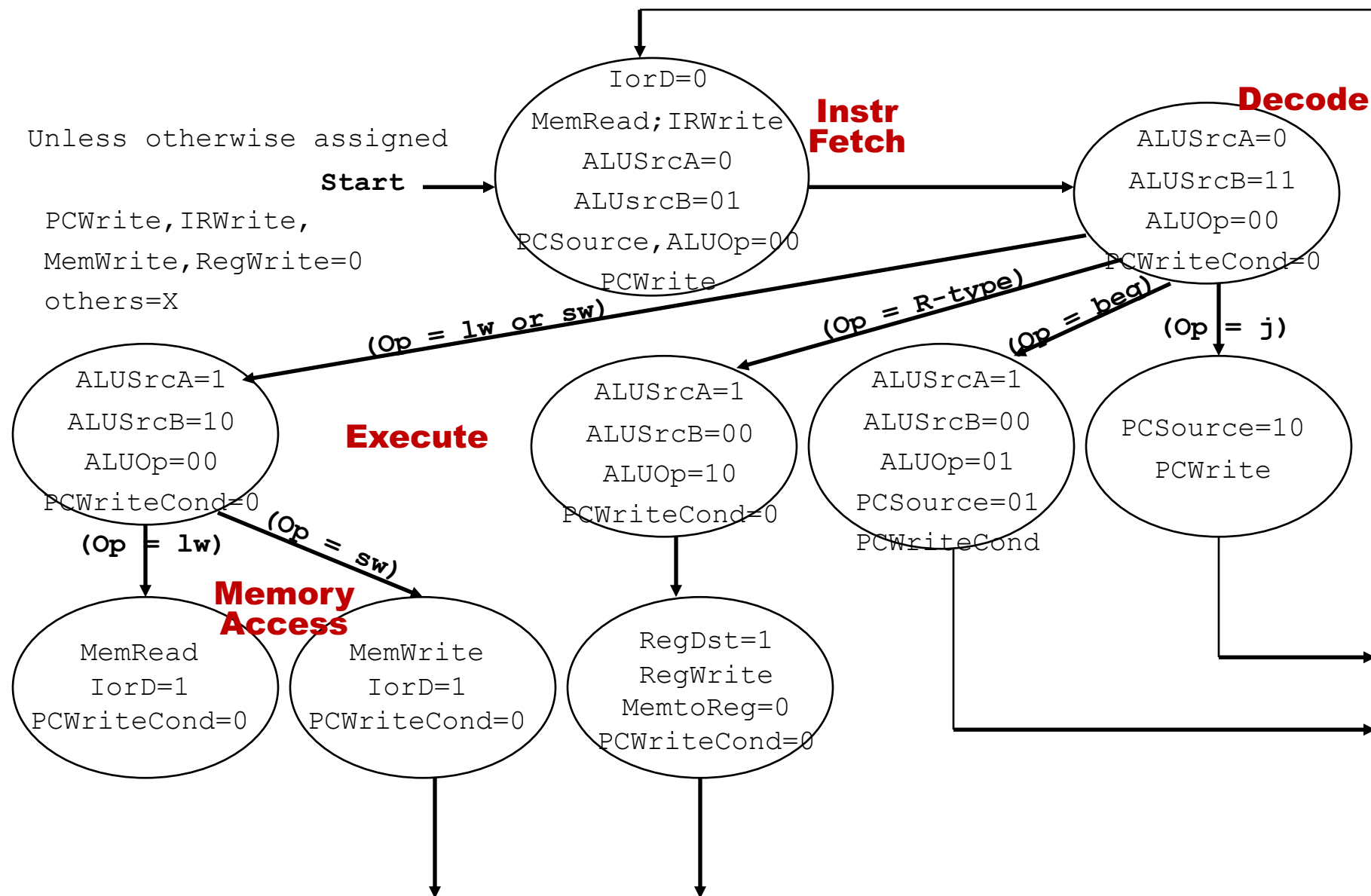


Step 5: Memory Read Completion (Write Back)

- All we have left is the write back into the register file the data just read from memory for lw instruction


$$\text{Reg}[\text{IR}[20-16]] = \text{MDR};$$

What about all the other instructions?

Datapath Activity During lw Write Back

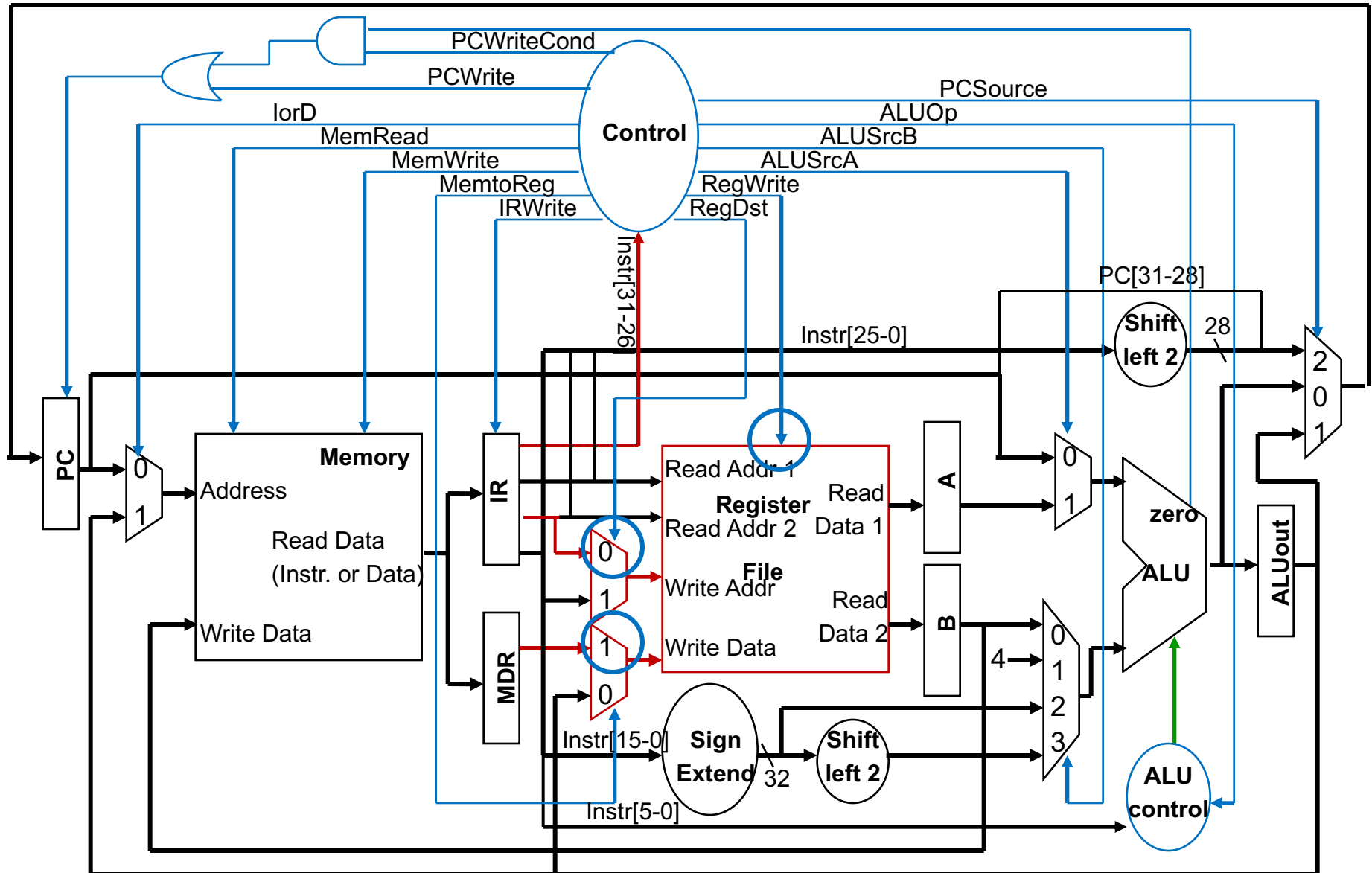

Write Back Control Signals Settings

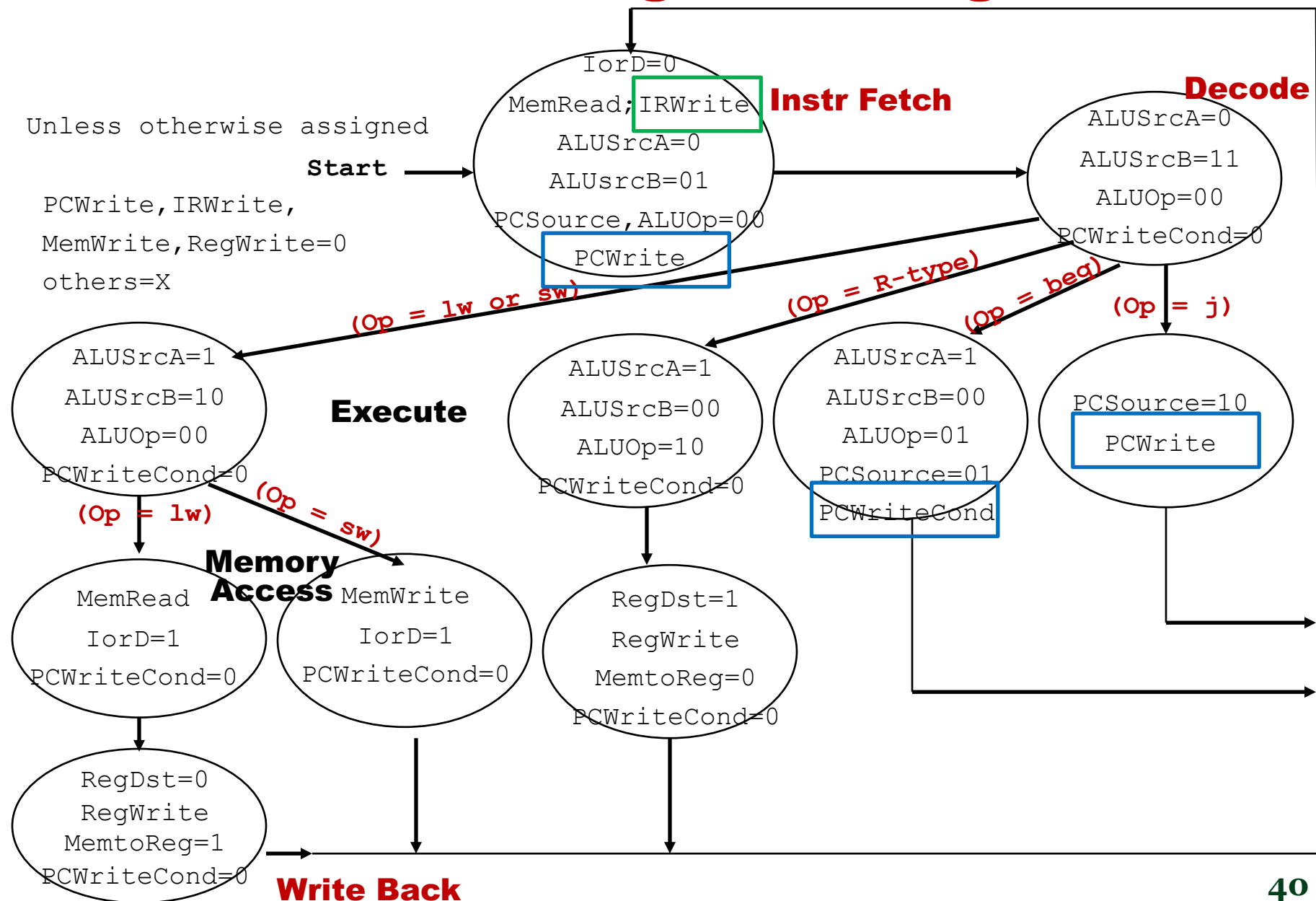

RTL Summary

Step	R-type	Mem Ref	Branch	Jump
Instr fetch	$IR = Memory[PC];$ $PC = PC + 4;$			
Decode	$A = Reg[IR[25-21]];$ $B = Reg[IR[20-16]];$ $ALUOut = PC + (sign-extend(IR[15-0]) \ll 2);$			
Execute	$ALUOut =$ $A \text{ op } B;$	$ALUOut =$ $A + sign-extend$ $(IR[15-0]);$	if $(A == B)$ $PC =$ $ALUOut;$	$PC =$ $PC[31-28]$ $ (IR[25-$ $0] \ll 2);$
Memory access	$Reg[IR[15$ $-11]] =$ $ALUOut;$	$MDR =$ $Memory[ALUOut];$ or $Memory[ALUOut]$ $= B;$		
Write- back		$Reg[IR[20-16]]$ $= MDR;$		

Example

Using the following instruction mix, what is the CPI, assuming that each state in the multicycle CPU requires 1 clock cycle?

Load	25%
store	10%
branches	11%
jumps	2%
ALU	52%