

# **Lecture 06: Memory Address Decoding**

# **Reference Book:**

## **The 80x86 IBM PC and Compatible Computers**


---

### **Chapter 10**

### **Memory and Memory Interfacing**

### **Chapter 11**



### **I/O and the 8255**

 
  
# Review on Memory Chips

---

- Key concepts: capacity, organization (the number of locations X the size of addressable unit), access time
- Packaging



# What to Learn?

---

- How does the 8086 CPU execute an instruction like **MOV BX, [1000h]**?
- What is the difference between executing **MOV BX, [1000h]** and executing **MOV [1001h], BX** ?
- What is the difference between accessing memory and accessing I/O devices?





# Memory Address Decoding

---

- According to **your instructions** that access memory
  - E.g., `MOV AX, [0012H]`
- **CPU** calculates the physical address of the operand and put corresponding signals on the address bus
  - E.g., if DS=0900H, *what's the PA?*
- **Memory address decoding circuitry** locates the specific memory chip that stores the desired data
  - Examine address decoding using logic gates and 74LS138 decoder chips

# Memory Address Decoding


PA of 0900:0012 = 09012H

    

 
# Quiz

---

What's the type and the address range of this memory chip?



# The 74LS138 Decoder Chip

 

Function Table


Inputs									
Enable	Select	Outputs							
G1G2	C B A	Y0	Y1	Y2	Y3	Y4	Y5	Y6	Y7
X H	X X X	H	H	H	H	H	H	H	H
L X	X X X	H	H	H	H	H	H	H	H
H L	L L L	L	H	H	H	H	H	H	H
H L	L L H	H	L	H	H	H	H	H	H
H L	L H L	H	H	L	H	H	H	H	H
H L	L H H	H	H	H	L	H	H	H	H
H L	H L L	H	H	H	H	L	H	H	H
H L	H L H	H	H	H	H	H	L	H	H
H L	H H L	H	H	H	H	H	H	L	H
H L	H H H	H	H	H	H	H	H	H	L


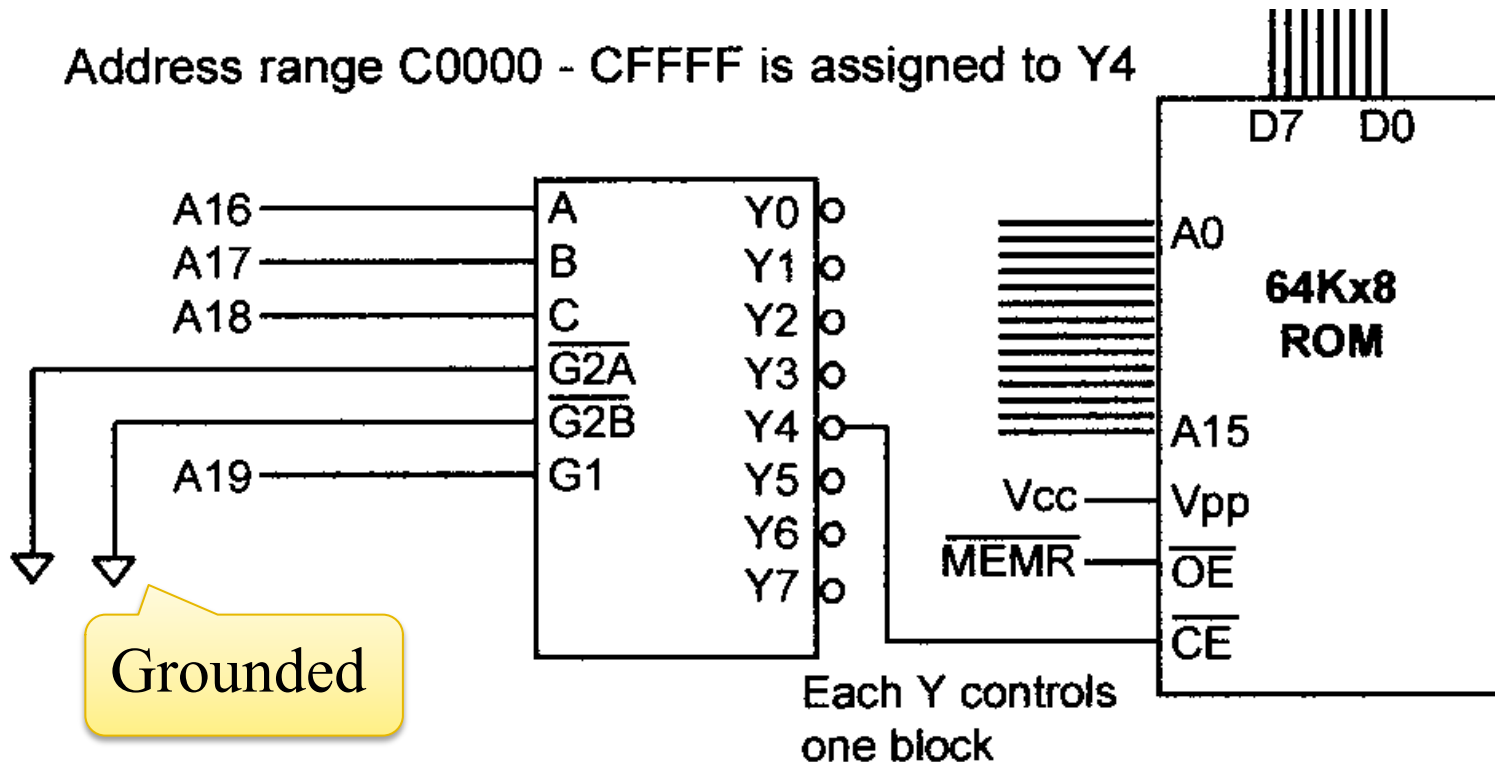
# Using 74LS138 to Decode

---


Address range C0000 - CFFFF is assigned to Y4



# Quiz 2

---

What's the address range for Y4 and Y7?

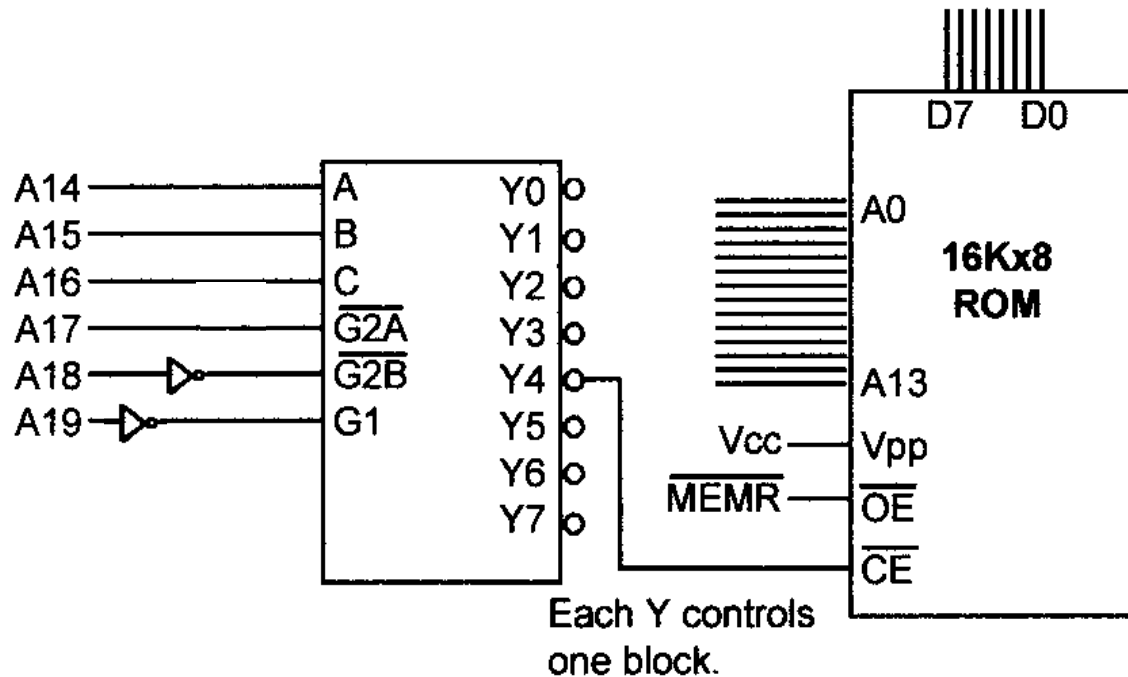

# More on Address Decoding

---

- Absolute address decoding
  - All address lines are decoded
- Linear select decoding
  - Only selected lines are decoded
  - Cheap
  - But with **aliases**: the same memory unit (I/O port) with multiple addresses
    - *Why does this happen?*

**Example 1.** In a particular computer, the address range from 0000h to 3FFFh is used for ROM, the range from 4000h to 5FFFh is reserved for future use, and the range from 6000h to 0FFFFh is used for RAM. Assume that the control signals for RAM are  $\text{CS}\sim$  and  $\text{WE}\sim$ , and the CPU has 16 address pins (i.e.,  $\text{A}_{15}\sim\text{A}_0$ ), 8 data pins (i.e.,  $\text{D}_7\sim\text{D}_0$ ), and  $\text{R}/\text{W}\sim$  and  $\text{MREQ}\sim$  control signals. Achieve the following requests.

- (1) draw the address decoding solution using a 74LS138 chip
- (2) if both ROM and RAM are built with  $8\text{K}\times 1$  memory chips, try to draw the connection between the CPU and the memory.
- (3) if ROM is built with  $8\text{K}\times 8$  memory chips and RAM is built with  $4\text{K}\times 8$  chips, try to draw the connection between the CPU and the memory.
- (4) what if ROM is built with  $16\text{K}\times 8$  memory chips and RAM is built with  $8\text{K}\times 8$  memory chips?

(1) draw the address decoding solution using a 74LS138 chip

### Solution.

The logic expression of each output of the 74LS138 chip:

$$\text{romsel0} = \overline{A_{15}} * \overline{A_{14}} * \overline{A_{13}} * \overline{\text{MREQ\#}}$$

$$\text{romsel1} = \overline{A_{15}} * \overline{A_{14}} * A_{13} * \overline{\text{MREQ\#}}$$


$$\text{ramsel0} = \overline{A_{15}} * A_{14} * A_{13} * \overline{\text{MREQ\#}}$$

$$\text{ramsel1} = A_{15} * \overline{A_{14}} * \overline{A_{13}} * \overline{\text{MREQ\#}}$$

$$\text{ramsel2} = A_{15} * \overline{A_{14}} * A_{13} * \overline{\text{MREQ\#}}$$

$$\text{ramsel3} = A_{15} * A_{14} * \overline{A_{13}} * \overline{\text{MREQ\#}}$$

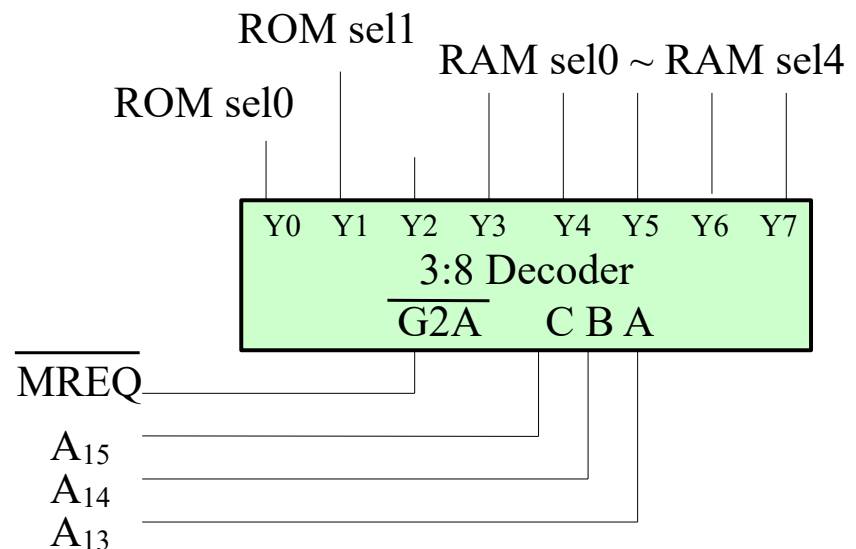
$$\text{ramsel4} = A_{15} * A_{14} * A_{13} * \overline{\text{MREQ\#}}$$



(2) if both ROM and RAM are built with  $8K \times 1$  memory chips, try to draw the connection between the CPU and the memory.


---

**Solution.**

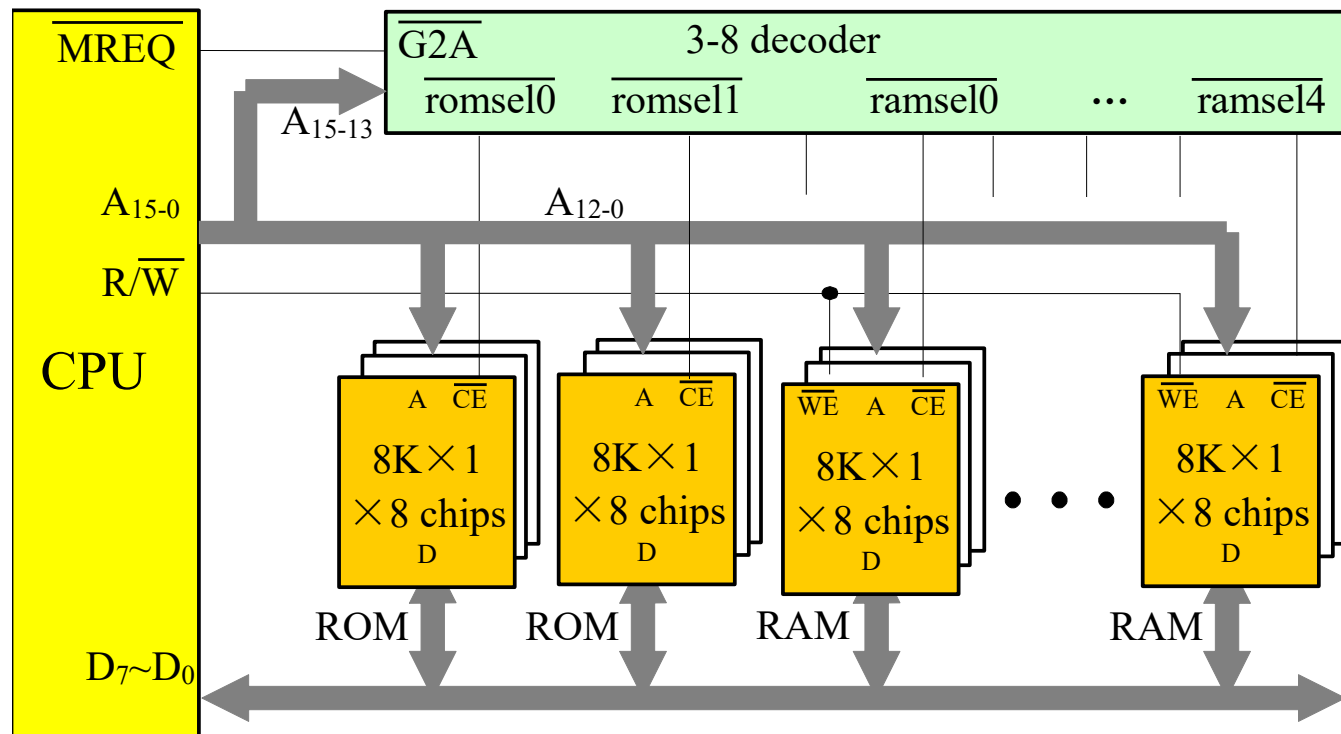


(3) if ROM is built with  $8K \times 8$  memory chips and RAM is built with  $4K \times 8$  chips, try to draw the connection between the CPU and the memory.

**Solution.**

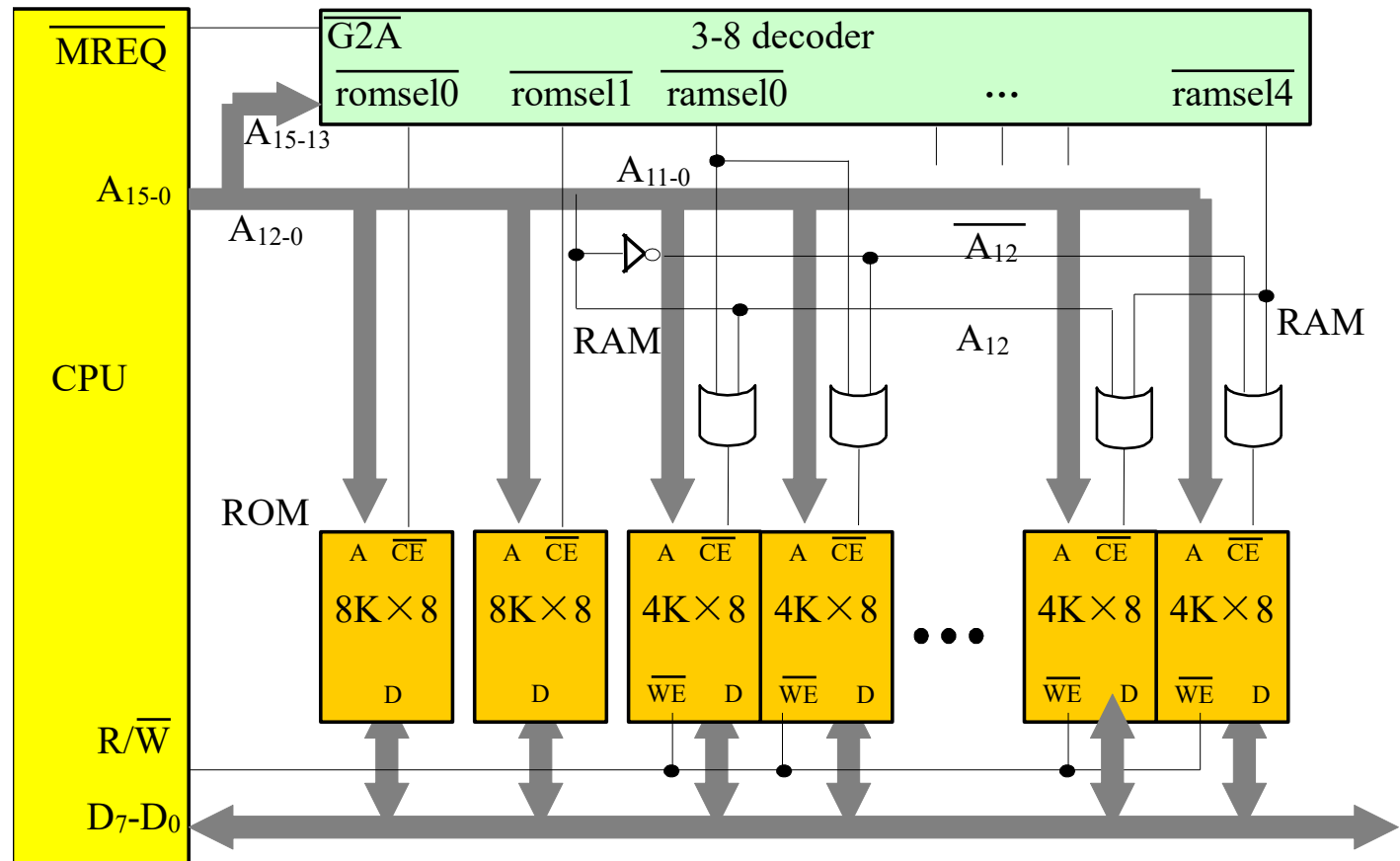

(4) what if ROM is built with  $16K \times 8$  memory chips and RAM is built with  $8K \times 8$  memory chips?

**Solution.**

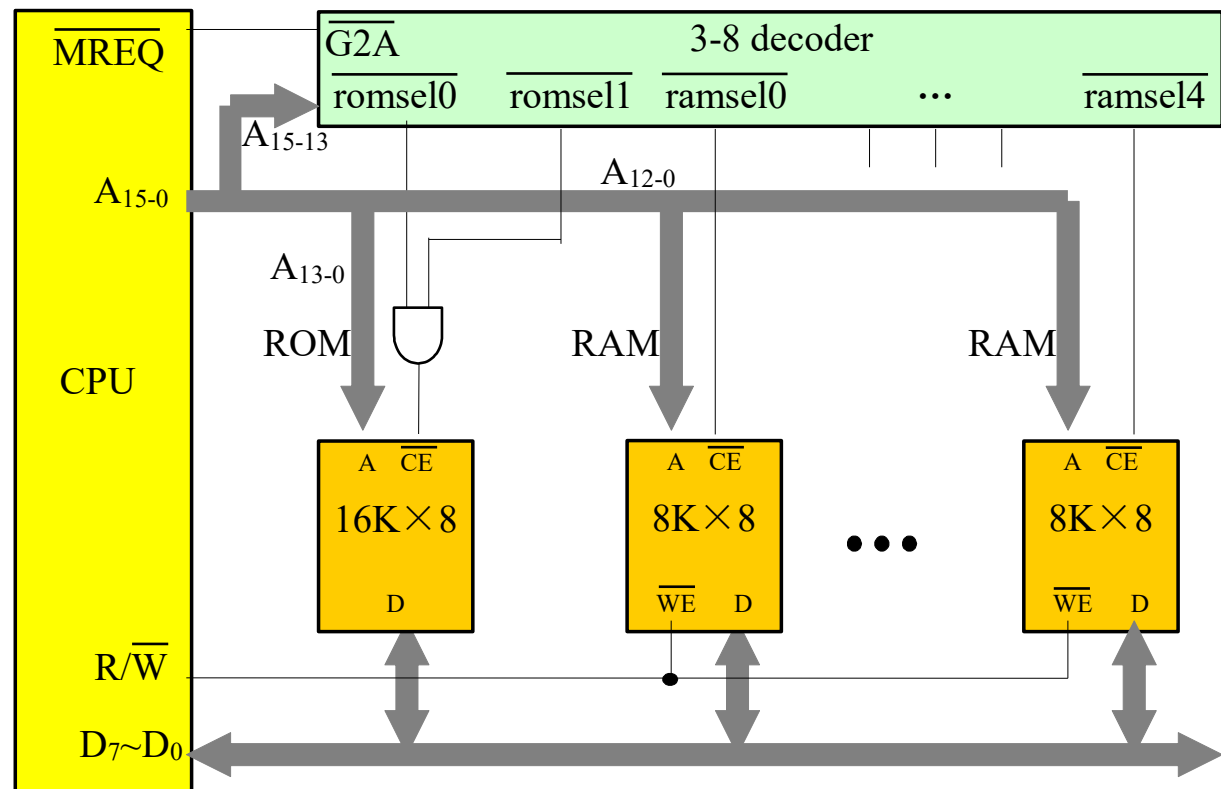




**Example 2.** Assume one computer system needs 512 byte RAM and 512 byte ROM. If RAM is built with  $128 \times 8$  memory chips and ROM is built with  $512 \times 8$  memory chips, please specify the address range of each memory chip. Given that RAM chips need  $\overline{CS}$  and  $\overline{WE}$  control signals, ROM chips need only  $\overline{CS}$  control signal, and the CPU has 16 address pins ( $A_{15} \sim A_0$ ), 8 data pins ( $D_7 \sim D_0$ ) and  $\overline{R/W}$  and  $\overline{MREQ}$  control signals, draw the connection between the CPU and the memory.

**Solution.** The address range of each memory chip:

Memory Chip	Address range (hex)	binary
RAM1	0000~007F	0 0 0 x x x x x x x
RAM2	0080~00FF	0 0 1 x x x x x x x
RAM3	0100~017F	0 1 0 x x x x x x x
RAM4	0180~01FF	0 1 1 x x x x x x x
ROM	0200~03FF	1 x x x x x x x x x

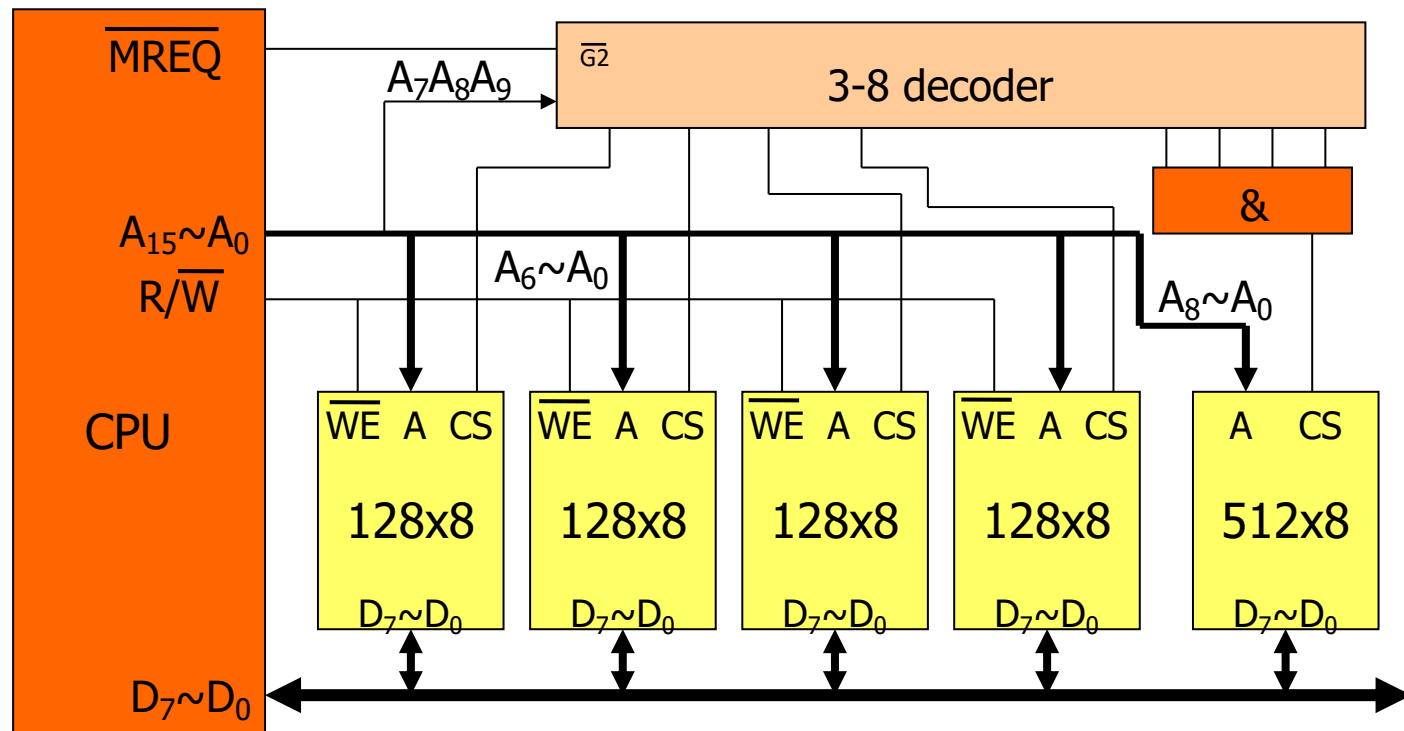As the total volume of the memory is 1K, we need 10 address lines. RAM chips need 7 address lines and ROM chips need 9 address lines.



# Data Integrity

---

- Checksum byte for ROM
- Parity bit for DRAM
- CRC for disks and the Internet

# Checksum Byte

---

- Check the integrity of a series of bytes
  - Calculation
    - | Add all bytes together and drop all carries
    - | Take the 2's complement of the sum
  - Store the checksum byte together with data
  - check the integrity by adding data and the checksum together
  - *Then how to prove the integrity of the data?*
  - E.g., 38H, 23H, 33H, 07H, what is the checksum byte?

6BH

# Parity bit


---

- Check the integrity of a series of bits (a byte)
  - even parity: if the number of 1s in the series of bits is odd, then the parity bit is set to 1; otherwise, set to 0, making the total number of 1s even (Data + the parity bit)
  - odd parity: if the number of 1s in the series of bits is odd, then the parity bit is set to 0; otherwise, set to 1
  - For PF in 8086, odd parity is used, i.e., if data have even number of 1s, the parity bit is set

# Memory Organization in 8086

## ■ Even and odd banks


BHE	A0		
0	0	Even word	D0 - D15
0	1	Odd byte	D8 - D15
1	0	Even byte	D0 - D7
1	1	None	

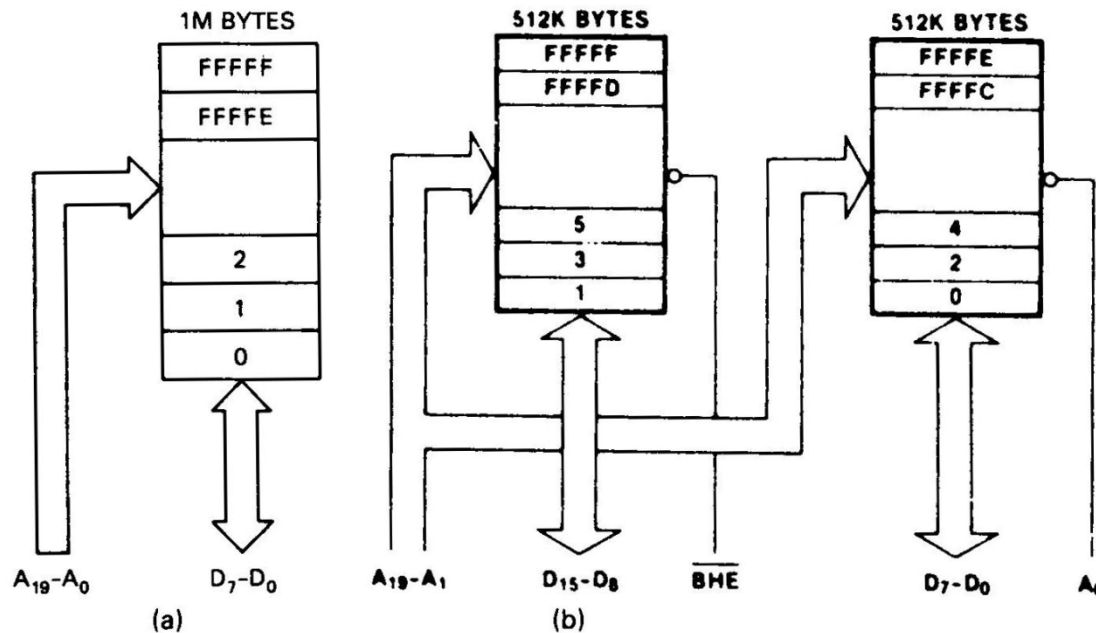

Address bits  $A_1$  through  $A_{19}$  select the storage location that is to be accessed. They are applied to both banks in parallel.  $A_0$  and bank high enable ( $\overline{BHE}$ ) are used as **bank-select** signals.

 
# Byte-Memory Operations

- Byte-memory operation at even address X



MOV AL, [100h]

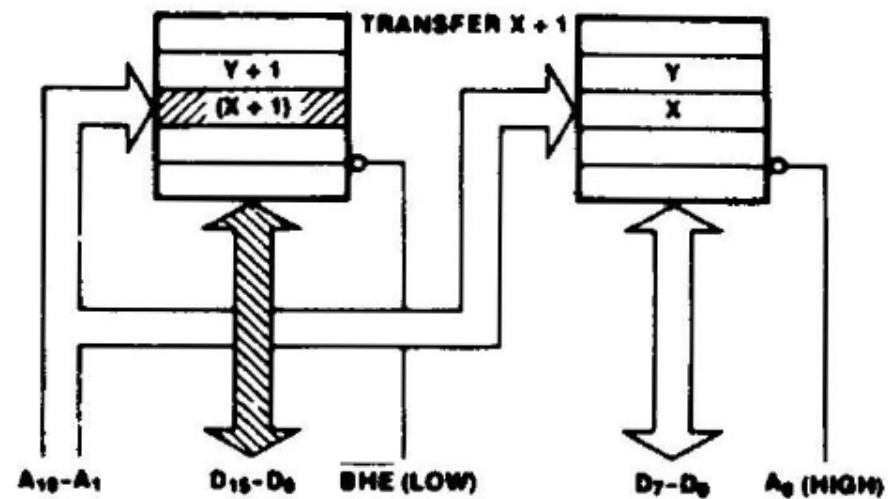
- Byte-memory operation at odd address X+1



MOV AL, [101h]
 
# Aligned Word-Memory Operations

- Accessing an **aligned word** at even address X




Both the high and low banks are accessed at the same time. Both  $A_0$  and  $\overline{BHE}$  are set to 0. This 16-bit word is transferred over the complete data bus  $D_0$  through  $D_{15}$  in just one bus cycle.

```
MOV AX, [100h]
```


 
# Misaligned Word-Memory Operations

- Accessing an **misaligned word** at odd address  $X+1$





Two bus cycles are needed. During the first bus cycle, the byte of the word located at address  $X+1$  in the high bank is accessed over  $D_8$  through  $D_{15}$ . Even though the data transfer uses data lines  $D_8$  through  $D_{15}$ , to the processor it is the **low byte** of the addressed data word. In the **second memory bus cycle**, the even byte located at  $X+2$  in the low bank is accessed over bus lines  $D_0$  through  $D_7$ .

```
MOV AX, [101h]
```
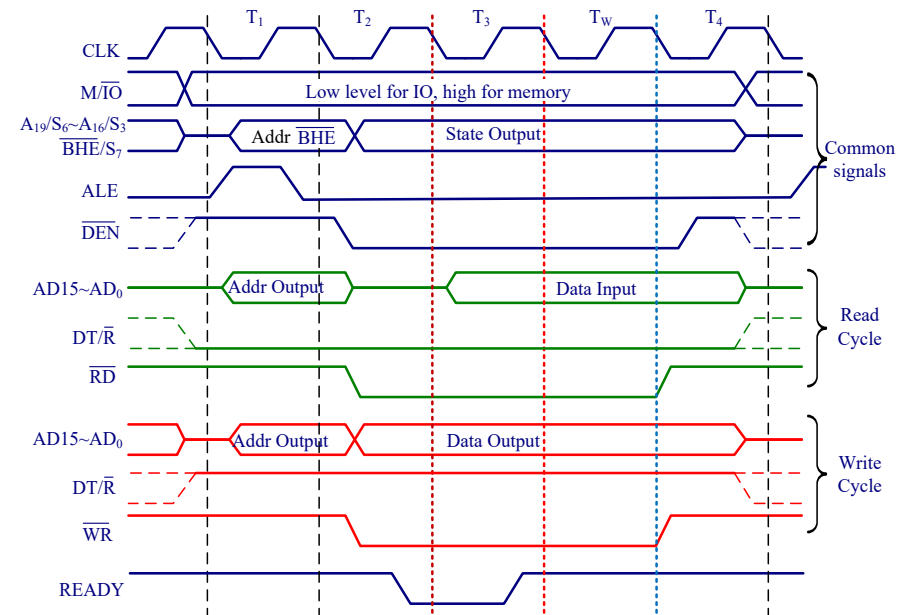 
# Let's Tell the Stories



Could you possibly tell the complete procedure of the 8086 CPU executing an instruction like **MOV BX, [1000h]**? What about **MOV [1001h], BX**?


  
# I/O in X86 family – The Other Space from Memory

---

- X86 microprocessors have an I/O space in addition to memory space
- Use special I/O instructions accessing I/O devices at **ports** (i.e., addresses for I/O)
- Memory can contain machine codes and data, I/O ports only contain data
- Also referred to as *peripheral I/O* or *isolated I/O*



# I/O Instructions – 8-Bit Instance

	<u>Inputting Data</u>	<u>Outputting Data</u>
Format:	IN dest, source	OUT dest, source

## ■ Direct I/O instructions:

- port# ranges from 00h to 0ffh, 256 ports in total

(1)	IN	AL, port#	OUT	port#, AL
-----	----	-----------	-----	-----------

## ■ Indirect I/O instructions:

- port# ranges from 0000h to 0ffffh, 65536 ports in all
- use a 16-bit address that resides in the DX register

(2)	MOV	DX, port#	MOV	DX, port#
	IN	AL, DX	OUT	DX, AL

- Note: no segment concept for port addresses

# I/O Example

---

In a given 8088-based system, port address 22H is an input port for monitoring the temperature. Write Assembly language instructions to monitor that port continuously for the temperature of 100 degrees. If it reaches 100, then BH should contain 'Y'.

## **Solution:**

```
BACK:      IN      AL, 22H
           CMP     AL, 100
           JNZ     BACK
           MOV     BH, 'Y'
```

# I/O Instructions – 16-Bit Instance

---

- For 16-bit I/O modules

- Direct I/O instructions:

  - port# ranges from 00h to 0ffh, 256 ports in total

IN AX, port#                      OUT port#, AX

- Indirect I/O instructions:

  - port# ranges from 0000h to 0ffffh, 65536 ports in all

  - use a 16-bit address that resides in the DX register

MOV DX, port#                      MOV DX, port#  
IN AX, DX    OUT DX, AX

# Interfacing 8-bit I/O Modules to a 16-bit Data Bus



---

- For 8086, data for even-address ports are carried on data bus D0-D7 and data for odd-address ports are carried on data bus D8-D15

<u>BHE</u>	<u>A0</u>	
0	0	Even-addressed words (uses D0 - D15)
0	1	Odd-addressed byte (uses D8 - D15)
1	0	Even-addressed byte (uses D0 - D7)
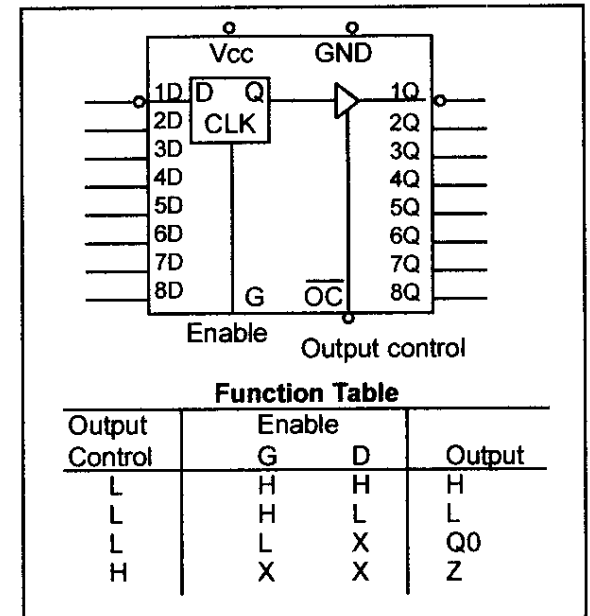 
# Output Port Design

- Latch the data coming from the CPU
- Address decoding





74LS373 D Latch

*What is the address of this port?*


 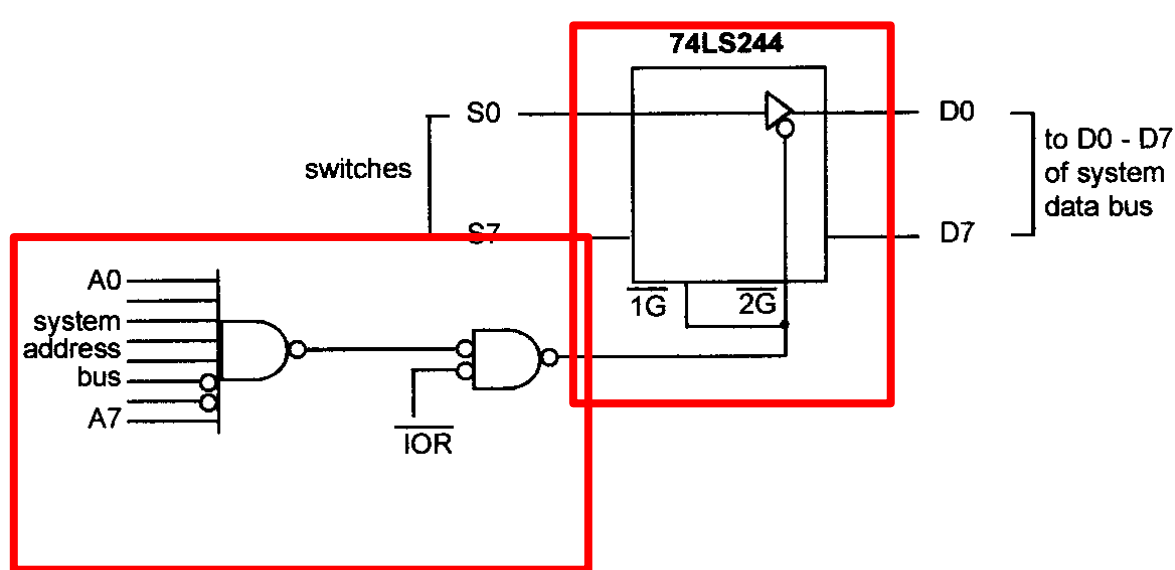
# Input Port Design

- Use *tri-state buffer* to connect to system data bus
- Address decoding



*What is the address of this port?*