

Lab 2 Content

- Master the connection between 8086 and 8255
 - I/O Address decoding
- Master the control word of 8255
- Use the 8255 in mode 0
 - As the input to read from 8 switches
 - As the output to turn on/off 7-segment LEDs
- Master the memory address mapping
 - How to assign addresses to a memory chip
- Understand the concept of even/odd address, high/low byte of data bus, and even/odd banks


For the 8255

- Determine the port number according to the circuits
- Determine the control word given the requirement of each port (A/B/C) in 8255
 - As the input to read from 8 switches
 - As the output to turn on/off 7-segment LEDs

1) Determine the port number

→ implicit ← 隐式
explicit
↓
显式

AD

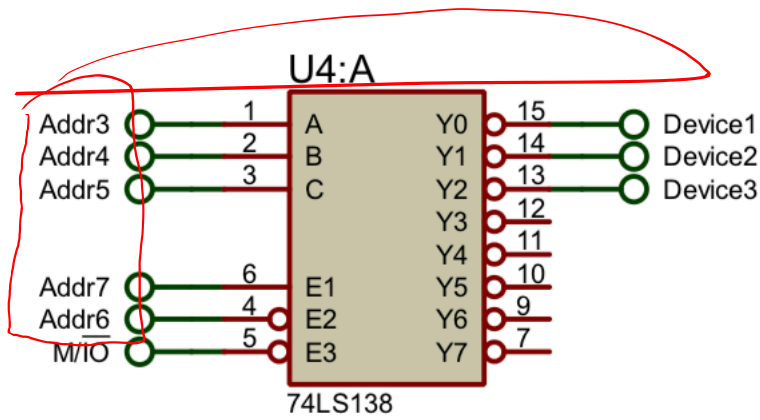

8255 Chip I/O Port Address Decoder Circuit


符号定义			
; 8255芯片端口地址 (Port number) 分配:			
PortA	EQU	90H	
PortB	EQU	92H	
PortC	EQU	94H	
CtrlPT	EQU	96H	

→
→
→
→

91H ←

IN/OUT

DATA 15-8

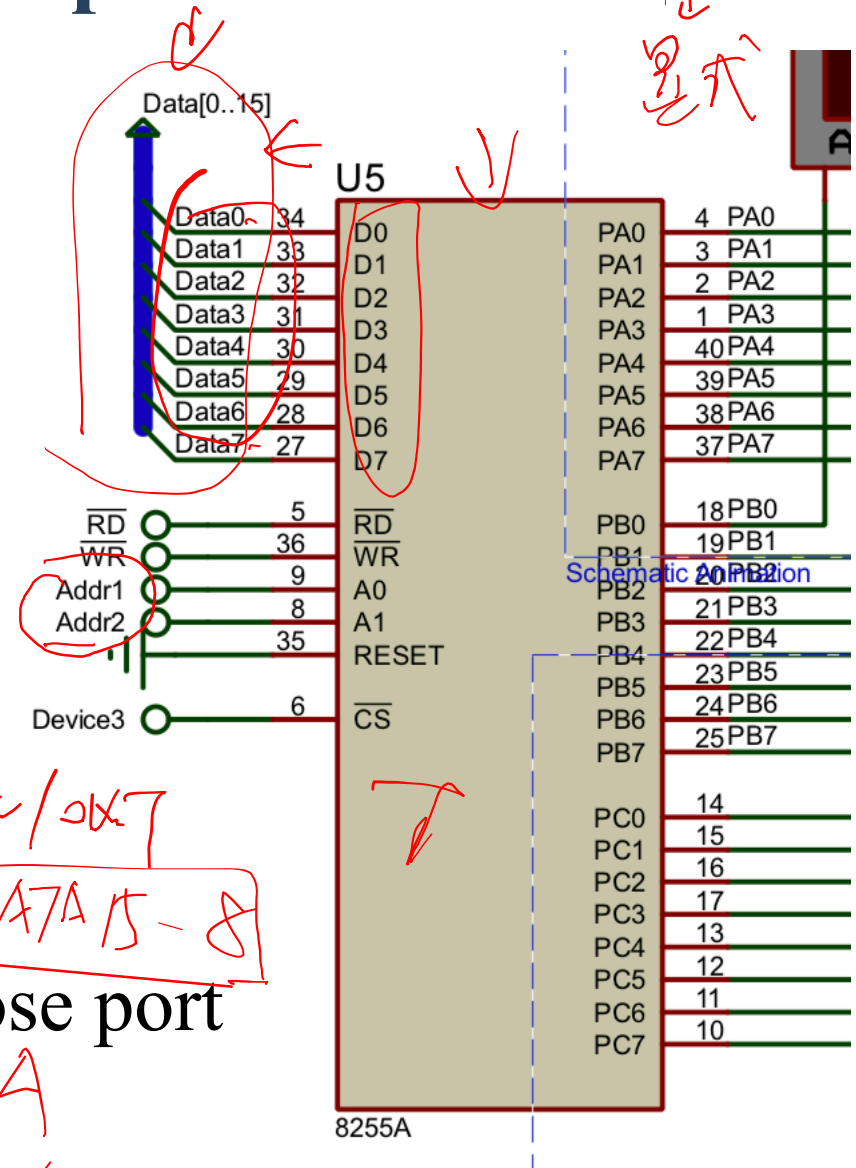


Schematic 20 PB2

➤ Quiz: how to derive those port numbers?

90H → A
91H → NO

2) Determine the control word

Cathode: 共阴极

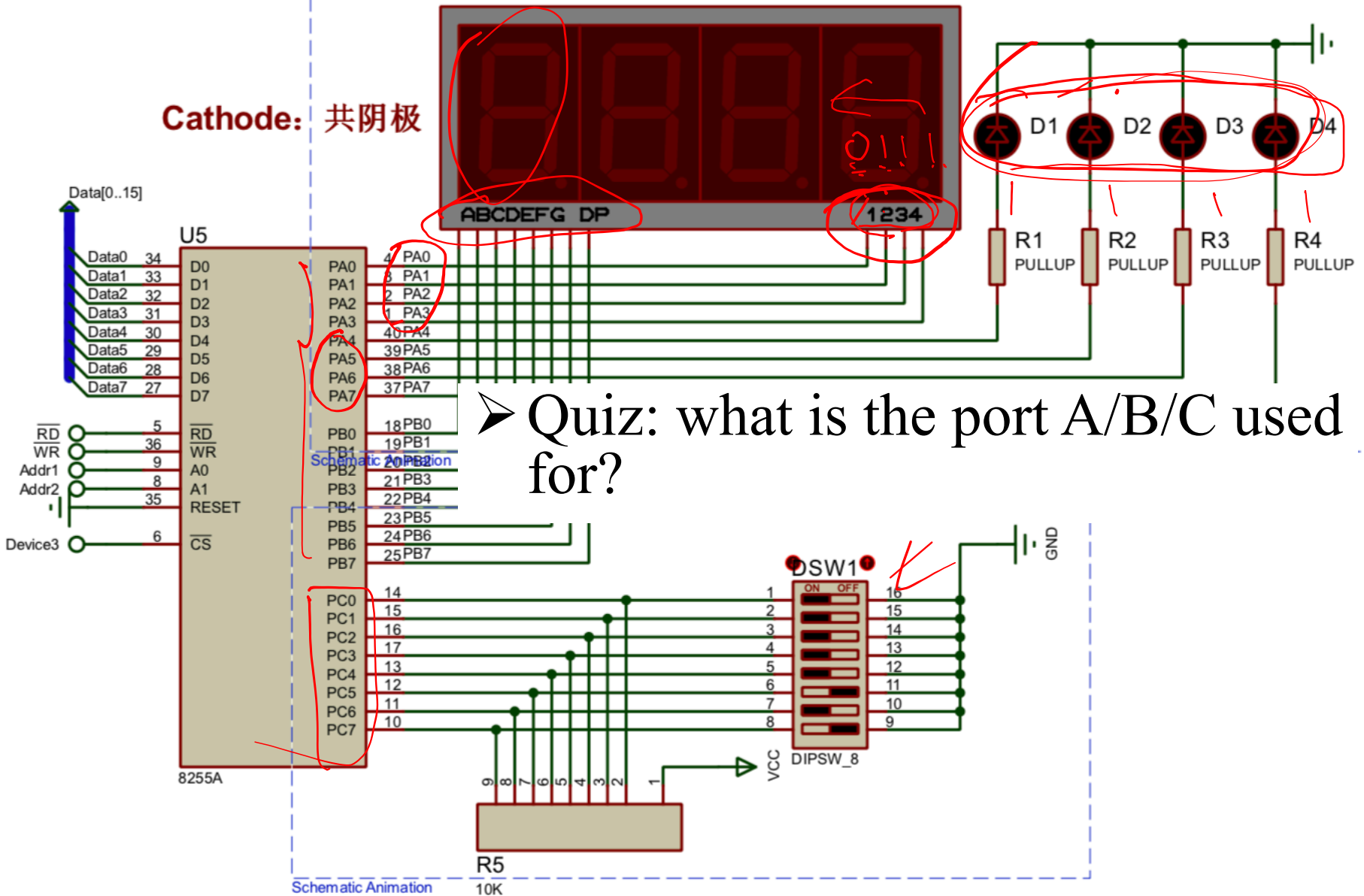

2) Determine the control word

```
;
; Init 8255 in Mode 0
; PortA Output, PortB Output
;
MOV AL,10000000B
OUT CtrlPT,AL ;
```

- Quiz: the example code configures A/B/C port as output; do we need to modify this?

How to drive the 7-segment LEDs

; SEGTAB是显示字符0-F，其中有部分数据的段码有错误，请自行修正

SEGTAB	DB 3FH ;	7-Segment Tube, 共阴极类型的7段数码管示意图
	DB 06H ;	
	DB 5BH ;	a a a -
	DB 4FH ;	f b
	DB 66H ;	f b
	DB 6DH ;	f b
	DB 7DH ;	g g g
	DB 07H ;	e c
	DB 7FH ;	e c
	DB 6FH ;	e c
	DB 77H ;	d d d h h h
	DB 7CH ;	
	DB 39H ;	b7 b6 b5 b4 b3 b2 b1 b0
	DB 5EH ;	DP g f e d c b a
	DB 79H ;	
	DB 7EH ;	

- Quiz: what's the purpose of the above table? Is there any mistakes in it?

How to drive the 7-segment LEDs

```

;-----
;      定义数据段
;-----
                .data
DelayShort      dw      4000
DelayLong       dw      40000
    
```

把数字1、2、3、4显示在数码管上

1111 1111

```

L1:
    MOV AL, 0FEh
    OUT PortA,AL
    MOV AL,SEGTAB
    OUT PortB,AL
    CALL DELAY

    MOV AL, 0FDh
    OUT PortA,AL
    MOV AL,SEGTAB + 1
    OUT PortB,AL
    CALL DELAY

    MOV AL, 0FBh
    OUT PortA,AL
    MOV AL,SEGTAB + 2
    OUT PortB,AL
    CALL DELAY

    MOV AL, 0F7h
    OUT PortA,AL
    MOV AL,SEGTAB + 3
    OUT PortB,AL
    CALL DELAY

    JMP L1
    
```

```

;-----
;      Delay system running for a while
;-----
DELAY PROC
    PUSH CX
    MOV CX,DelayShort
D1:   LOOP D1
    POP CX
    RET
DELAY ENDP
    
```


- Quiz1: what would happen if we comment the “CALL DELAY” instruction in the code?
- Quiz2: what would happen if we change the value of DelayShort variable?

Programming Requirement

➤ 1) 8255 part



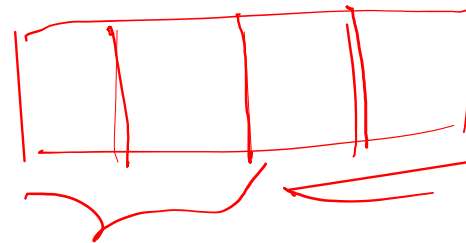
- c) Modify the demo program so that it takes the switches as input, displays the binary status of those switches connected to PC4-PC7 using LED lights D1-D4, and displays the hex value of the rest four switches connected to PC0-PC3 on the first digit of the LED display;
- d) Write a program so that it shows the hex value of PC4-PC7 switches on the first and third digits of the LED display, shows the hex value of PC0-PC3 switches on the second and fourth digits of the LED display, and controls the D1-D4 LED lights with PC4-PC7 switches.
- e)* Modify the schematic so that the data pins of 8255 connect to D8-D15 of the system bus, and repeat requirements b)-d).



Programming Requirement

➤ 1) 8255 part

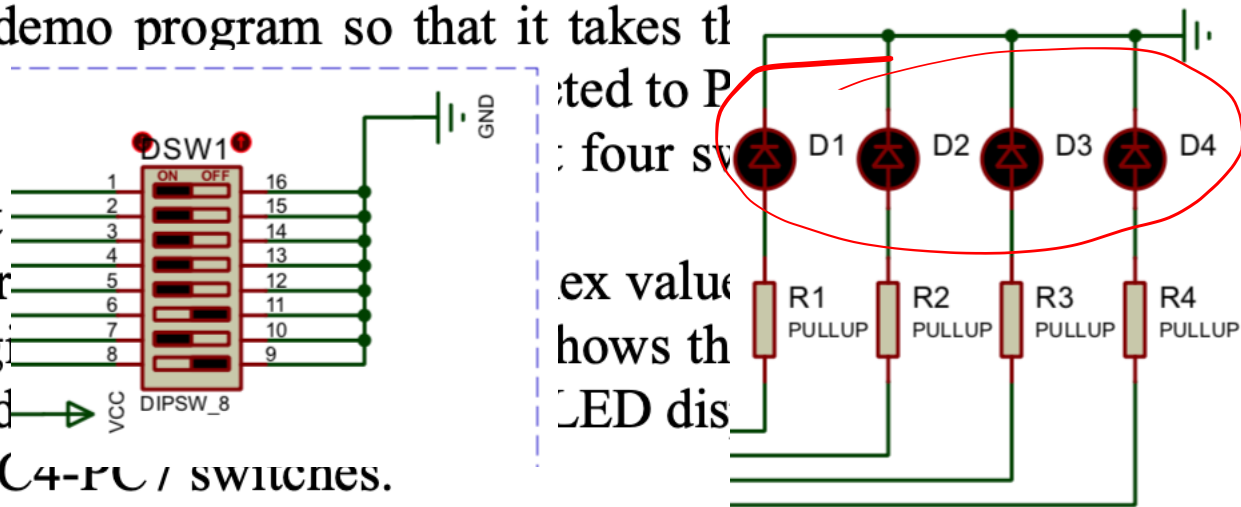- c) Modify the demo program so that it takes the binary status of the four switches connected to PC4-PC7 and displays the first digit on the second LED display.
- d) Write a program that reads the status of the four switches and displays the first digit on the second LED display.
- e)* Modify the schematic so that the data pins of 8255 connect to D8-D15 of the system bus, and repeat requirements b)-d).





- Read the switch status
- Turn on/off 7 segment LEDs correspondingly
- Turn on/off the four colorful LEDs

Programming Requirement

➤ 2) memory module part

- How to determine the memory range for each chip
- How to decide even/odd banks
- How to write to the given address range

Memory Module Design

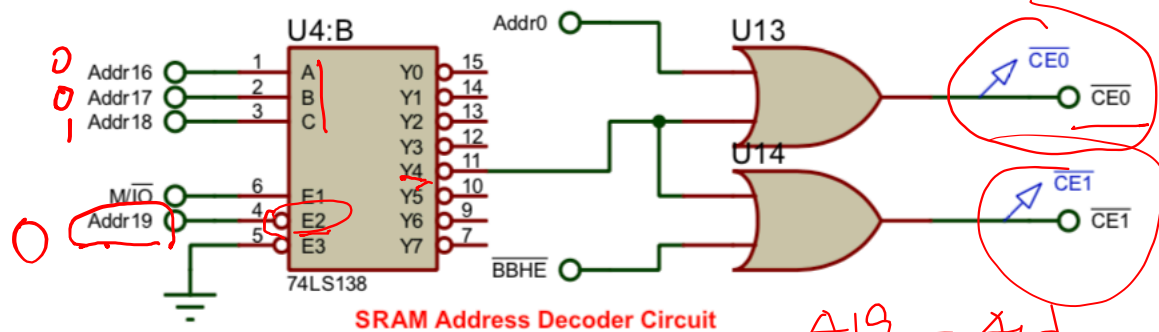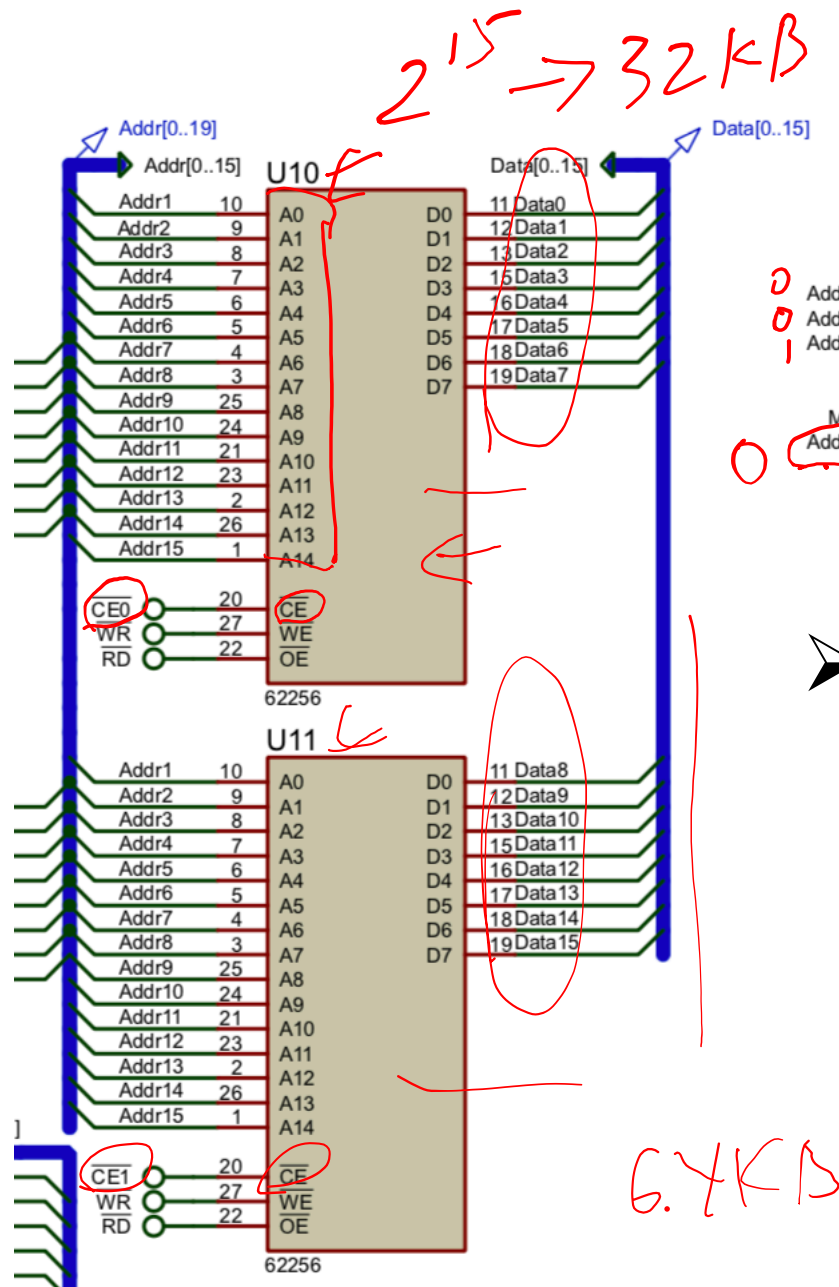

➤ Quiz: how to decide the memory address range of U10 and U11? How to decide the segment address for data segment?

```
MOV AX, 4000H
MOV DS, AX
MOV BX, 0H
```

4000H


+64KB

414

4000H

0100

A19-A17

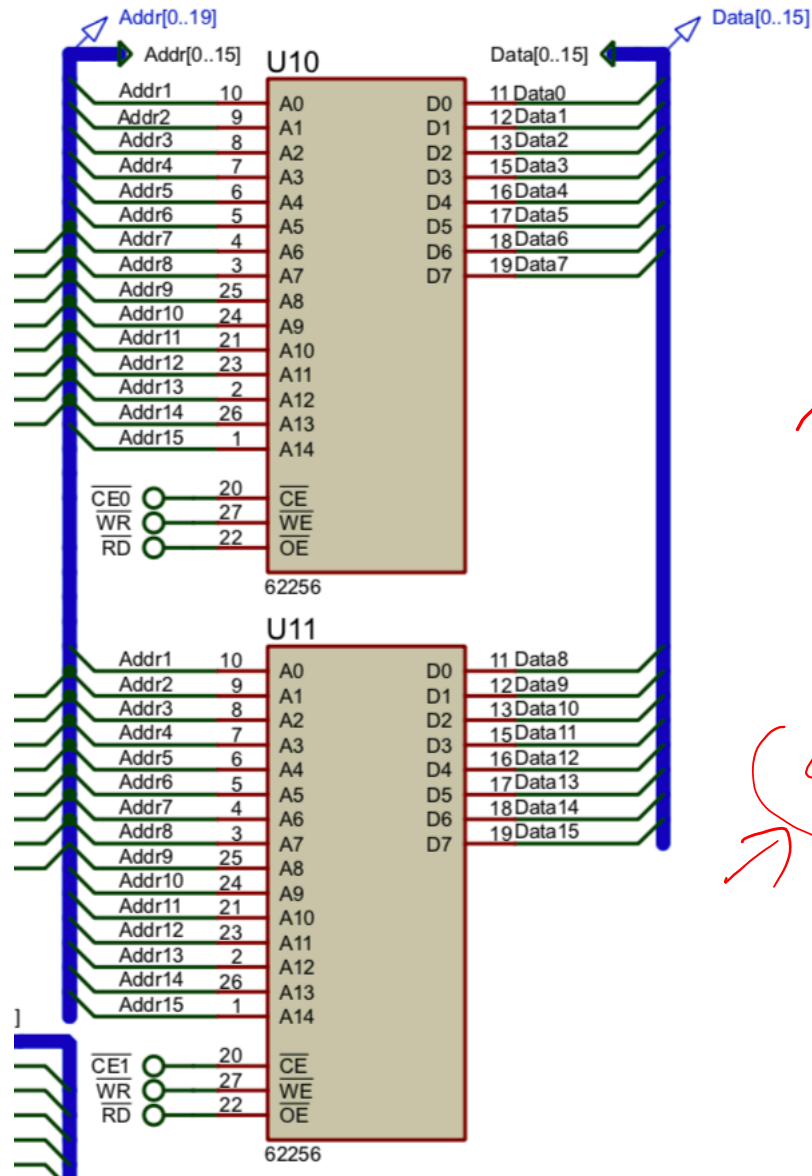

Quiz:

What is the address in the U10?

【the even or odd address in xxxxH-xxxxH (64KB)】

(4000H + 64KB)

What about U11?

The Error in the Example Code

- MOV **BYTE PTR** [BX],0FFH
- MOV [BX],0FFH
- Quiz: if we want to write a byte to the address, which instruction is correct and why?
 - How does the assembler know the size of memory access?

Programming Requirement

- b) ~~Compile~~ and run the `memory_extension_demo.asm` program. You should be able to observe the content of those two 62256 chips (i.e., U10 and U11 in the diagram). Specifically, after running the demo program for a while, pause the execution of the program and check the memory content by select the “Debug” menu and select “Memory Contents –U10” and “Memory Contents –U11”. Now you are asked to write a program which uses byte-memory operation to write odd numbers (e.g., 1, 3, 5 ...) into odd address bytes and even numbers (e.g., 0, 2, 4 ...) into even address bytes. Check with your results using above method;
- c) Modify the original schematic so that the address range of U10 an U11 starts from 80000h and repeat the above requirement b).
- d)* Write a program to use word-memory operation to fill those memory chips with value 66BBh.

➤ Simple loop that we have done before!