

# Lab 1 Content

➤ Install and run Proteus simulation software

6 Instructions:

<https://www.jianshu.com/p/21ad26e0d579>

o Download from jbox:

<https://jbox.sjtu.edu.cn/l/TnaRjS>



➤ Master the basic I/O operations in 8086

➤ Address decoding: how to derive the I/O port number given the address decoding circuitry

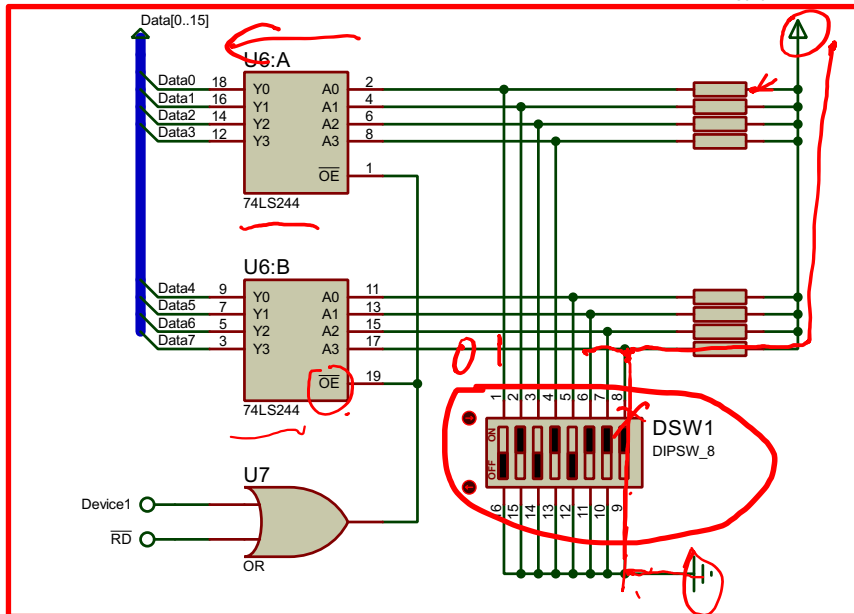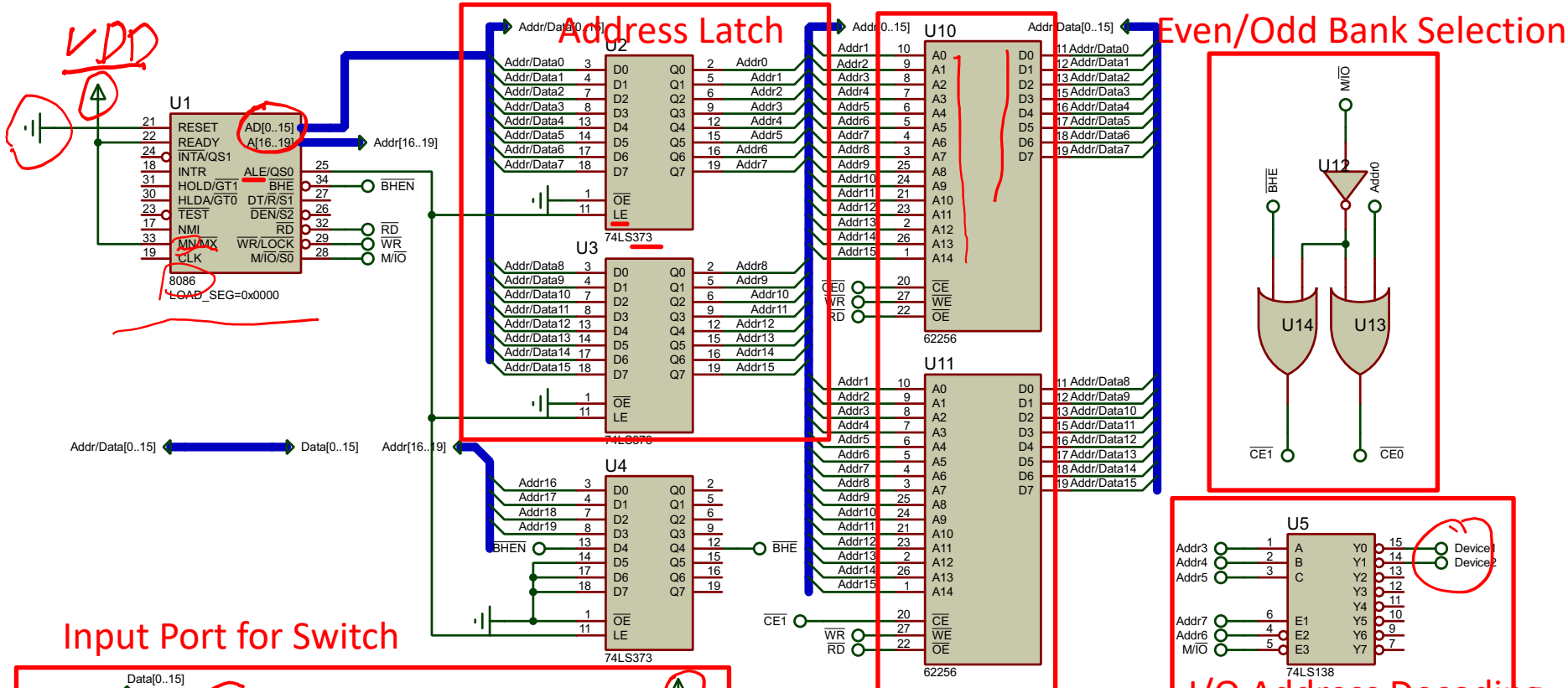
# Example Code

- The example code reads from the Device1 port
- Invert the value
- Write the new value to Device2
- Try running the code and change the switch status (Device1)


```
.MODEL SMALL
.DATA
.STACK 64
.CODE
Device1 EQU 80h
Device2 EQU 88h
main proc far
Again: IN AL, Device1
      NOT AL
      OUT Device2, AL
      JMP Again
main endp
END main
```



# Address Data Bus Decoupling

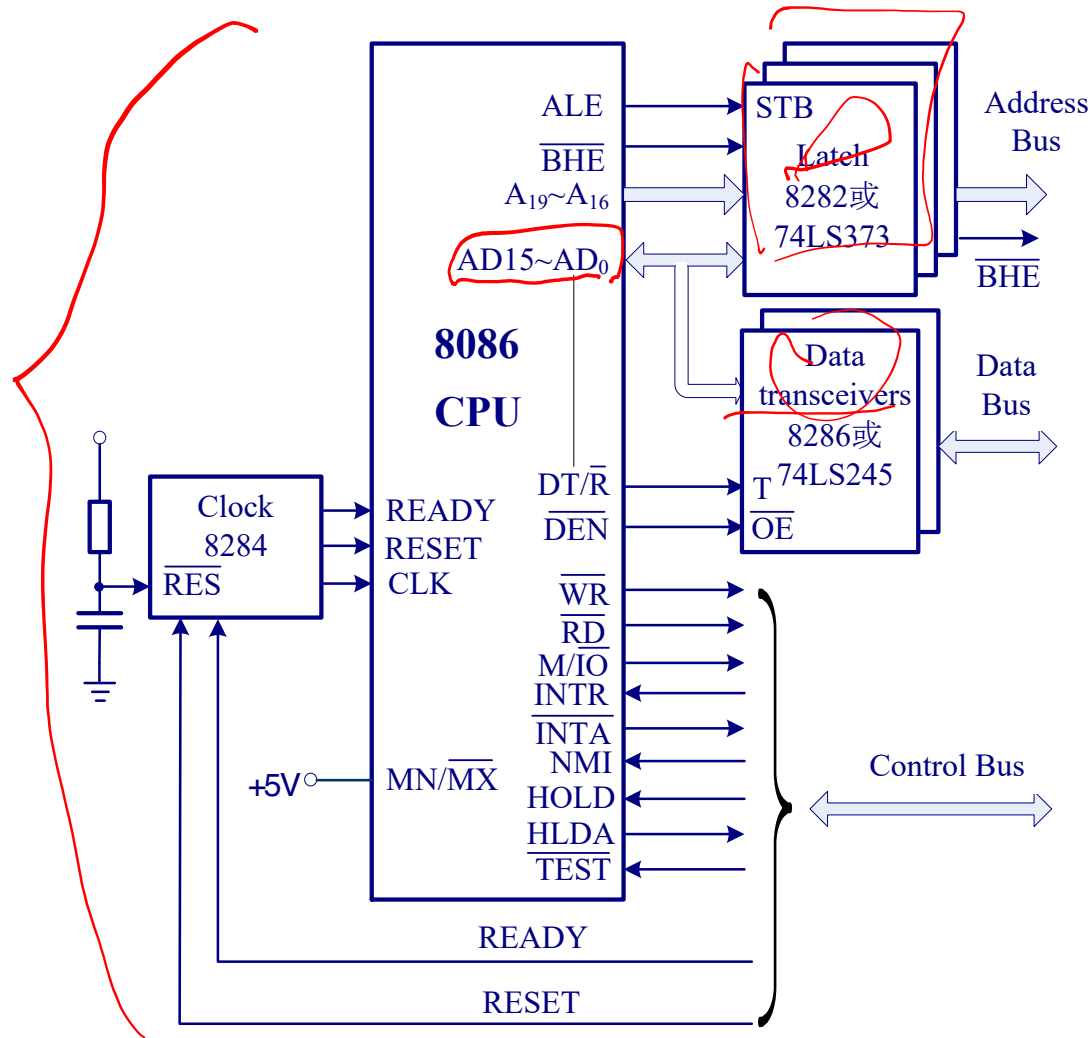

# Address Data Bus Decoupling

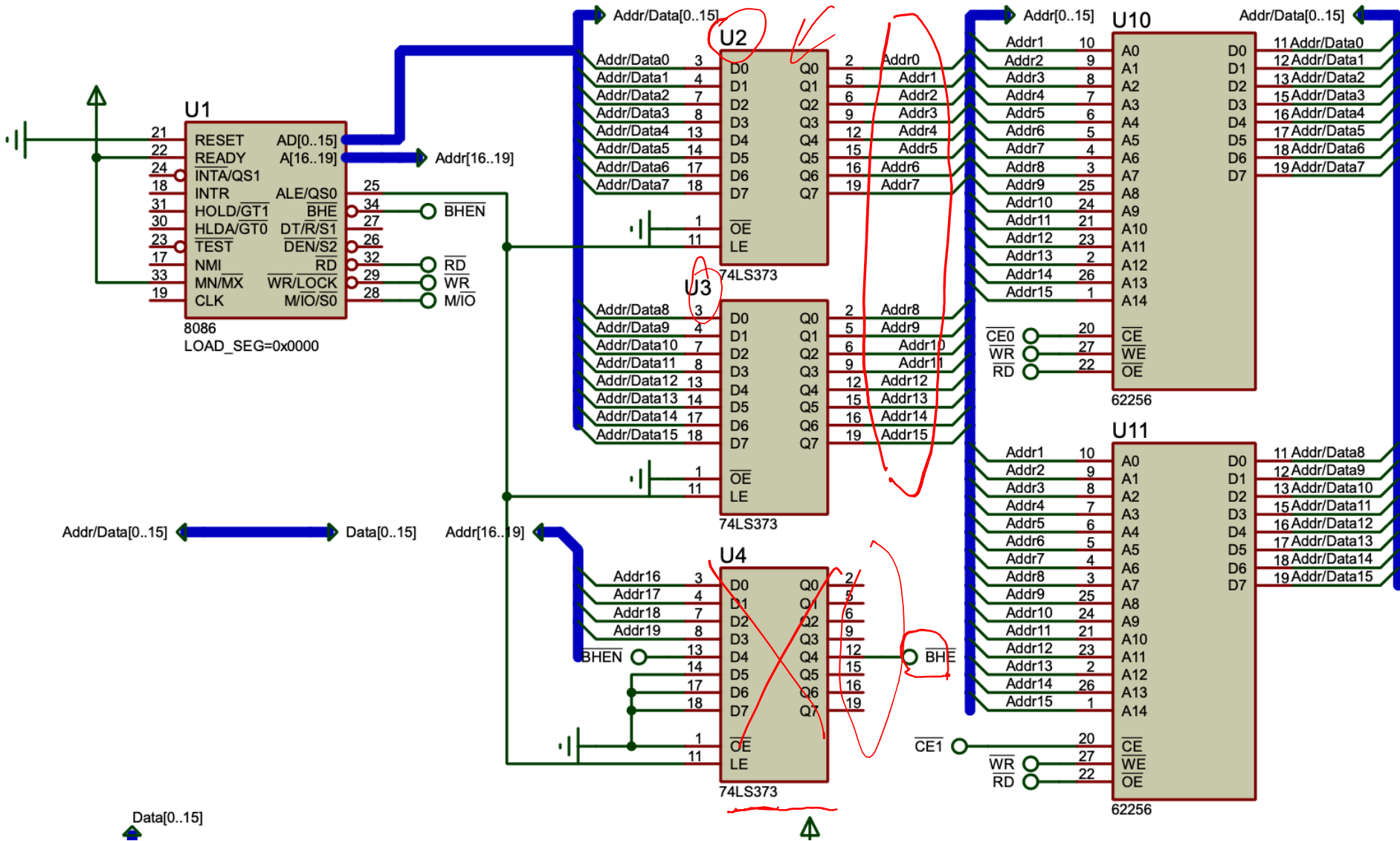


# Even/Odd Bank Selection

➤ When is CE1 and CE0 effective?


- $CE1 == 0$  needs  $BHE == 0$  and  $M/IO == 1$

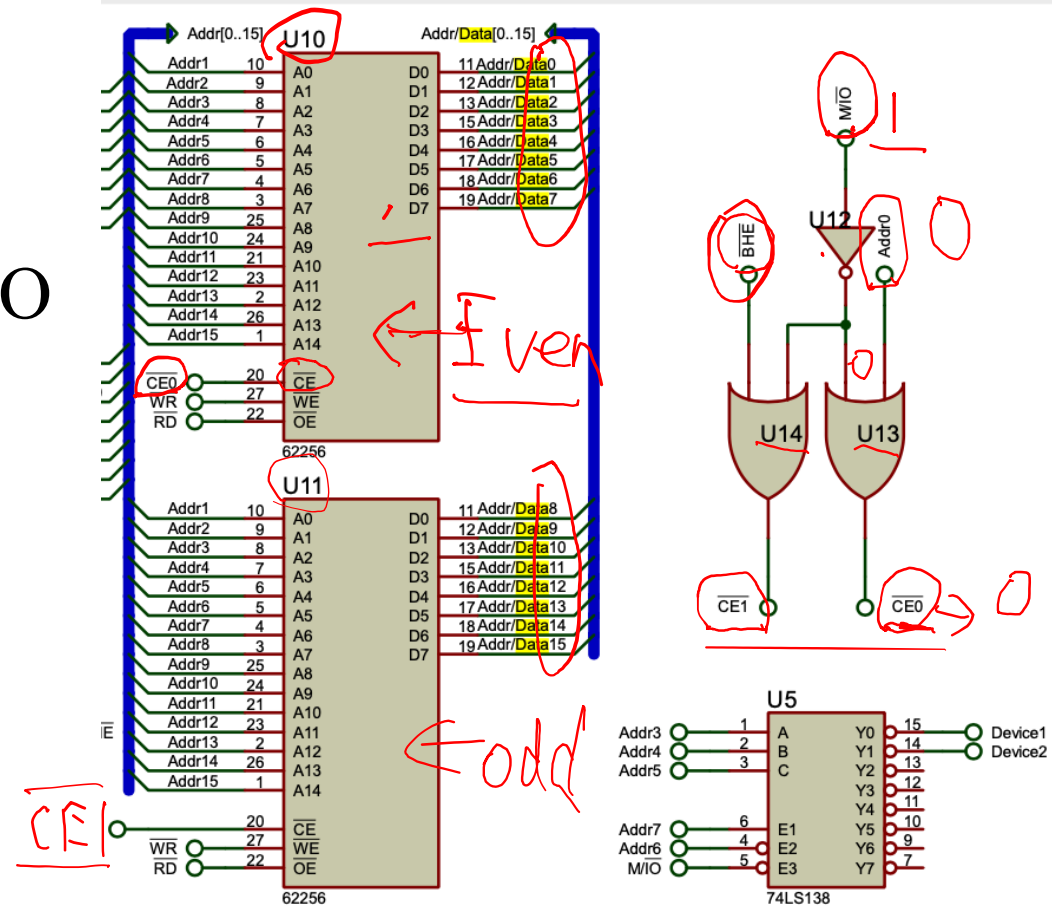- $CE0 == 0$  needs  $Addr0 == 0$  and  $M/IO == 1$


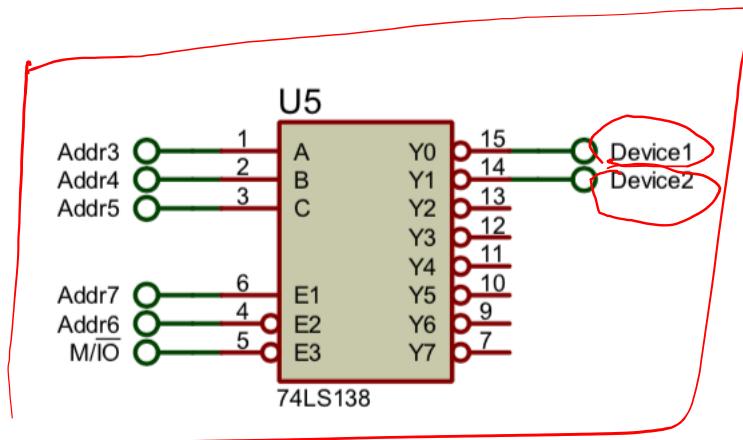
# I/O Address Decoding

- What addresses would generate the effective Device1 and Device2 signals?



# I/O Address Decoding


$$M \cdot V \rightarrow \underline{M/\overline{IO}} = 1$$
$$\underline{IN/OUT} \rightarrow \underline{M/\overline{IO}} = 0$$

## ➤ When Device1 is activated

- $\underline{M/\overline{IO}} = 0$ ,  $\underline{Addr7 = 1}$ ,  $\underline{Addr6 = 0}$ ,  $\underline{Addr5-3 = 000}$
- Port number 80H meets this requirement, but Device1 has more aliases
- Linear selective decoding, 部分译码
 
## ➤ When Device2 is activated


- $M/\overline{IO} = 0$ ,  $Addr7 = 1$ ,  $Addr6 = 0$ ,  $Addr5-3 = 001$
- Port number 88H meets this requirement, but Device2 has more aliases




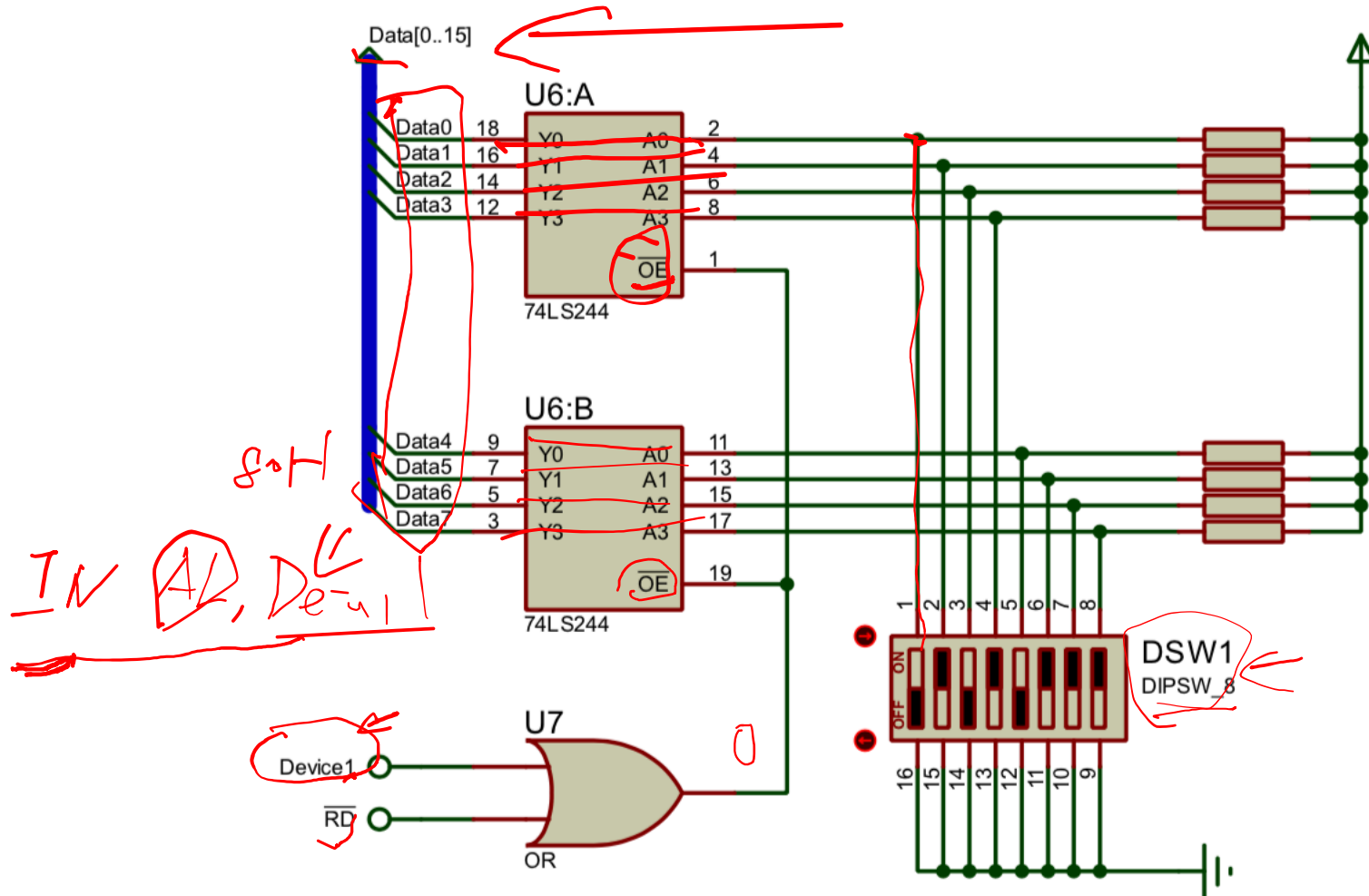
# Input Port Design

➤ How does the CPU reads from the switch?



## 思考题


➤ How does the CPU reads from the switch?

○ Through executing “IN AL, 80H” instruction

- Device1 is active
- The status of the switch is connected to the data bus D7-D0
- CPU reads D7-D0 to AL
- If the switch is ON (OFF), the corresponding bit is 0(1)
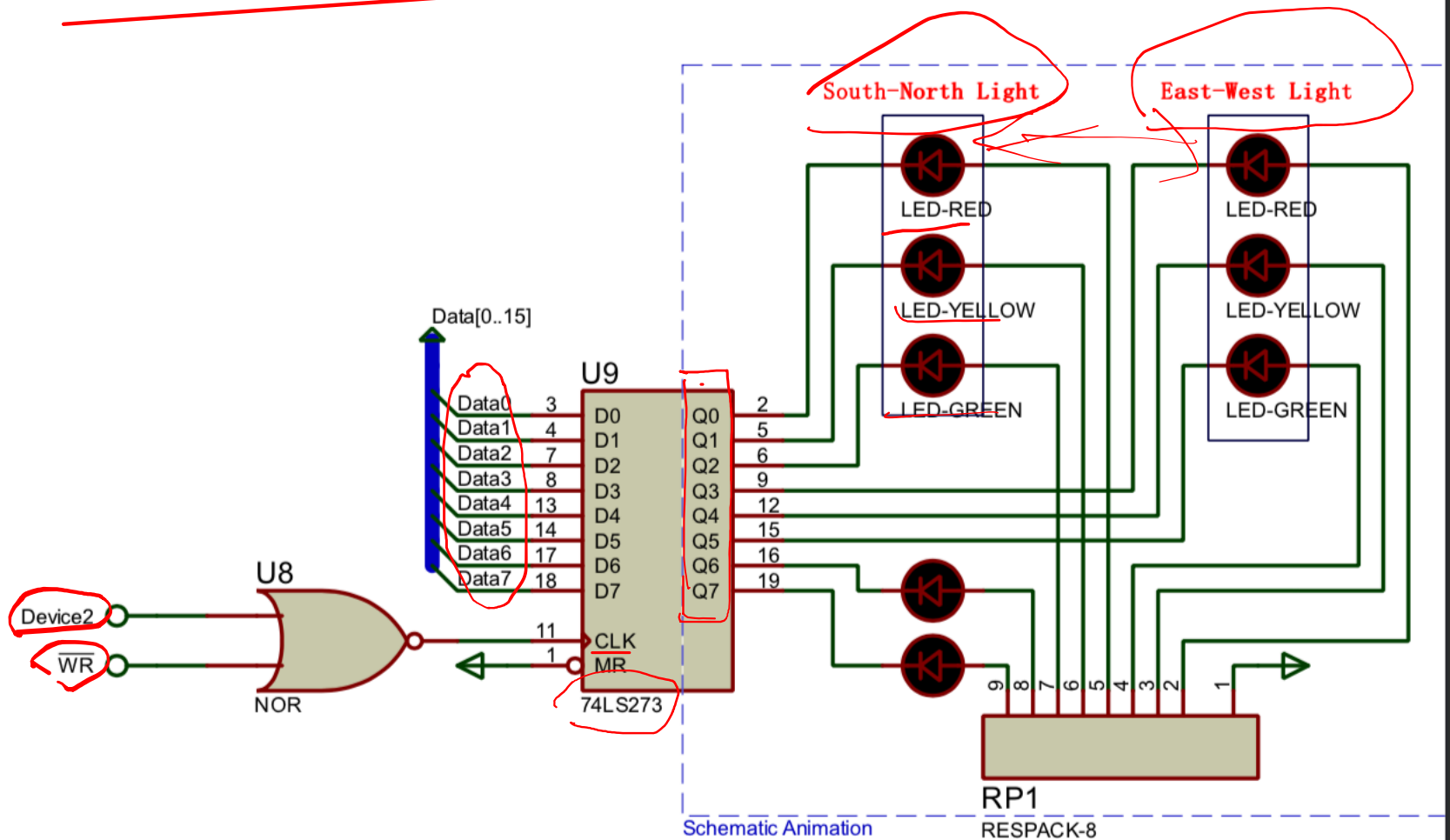
# Output Port Design

➤ How does the CPU control the LED light?



# Output Port Design

- How does the CPU control the LED light?
  - Through executing “OUT 88H, AL” instruction
    - Device2 is active
    - The value of AL is put on the data bus D7-D0
    - The latch (74LS273) records the values on D7-D0 and uses it to drive the eight LEDs
    - Value 0 turns the LED on, and value 1 turns the LED off
    - If the switch is ON (OFF), the corresponding bit is 0 (1)
    - Since we use the latch to store the 8-bit value, the status of LEDs do not change until a new value is written

# Requirement for This Programming Lab


- Write an assembly program to control the  
LEDs with three lights (red, green, and yellow),  
which mimics the traffic light

# nt for This Programming Lab

sembly program to control the  
hree lights (red, green, and yellow),

The state of port 273

State	Meaning	The state of 273 D7---D0
<u>State 0</u> ←	<u>Both directions are red</u>	<u>× × 110110 36H</u>
<u>State 1</u>	South-north green, east-west red	<u>× × 110011 33H</u>
<u>State 2</u>	South-north green blinks then yellow, east-west red	South-north green blinks (on and off), east-west red:

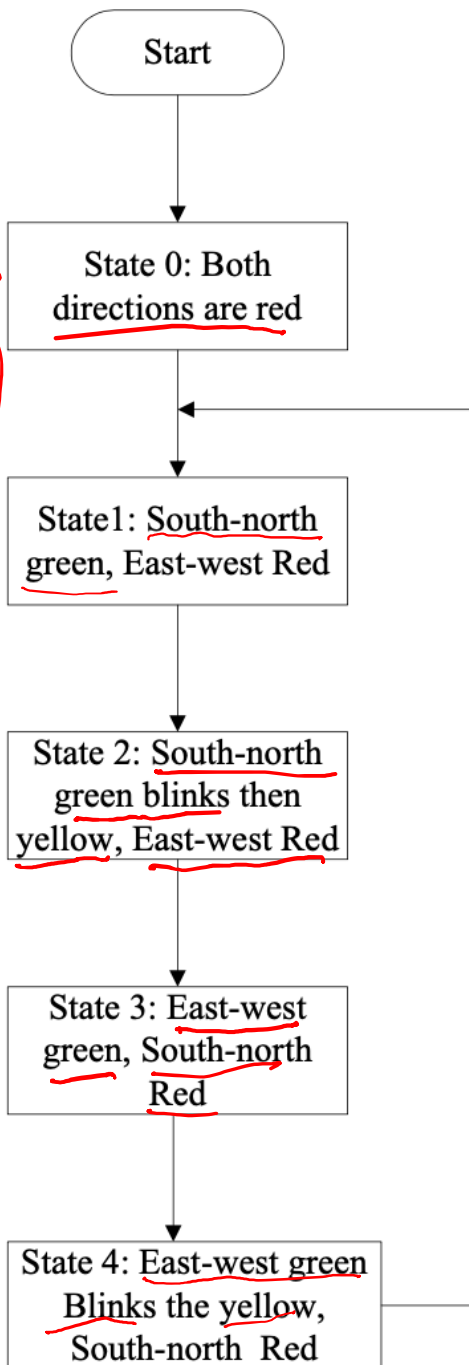

## Requirement II

➤ How should we change the I/O address decoding circuitry to

- Device1 corresponds to 90H
- Device2 corresponds to A0H

